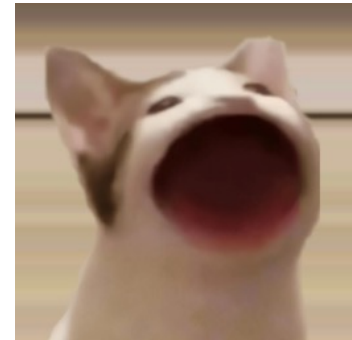


Memory II, FSMs, Pipelining

6.205 Fall 2024


Memory Example!

- In the first part of week 05 you're going to be displaying popcat on your FPGA over video.
- We need to store popcat
- Popcat is a 256X256 24 bit color image.
- How to encode with memories?



Popcat

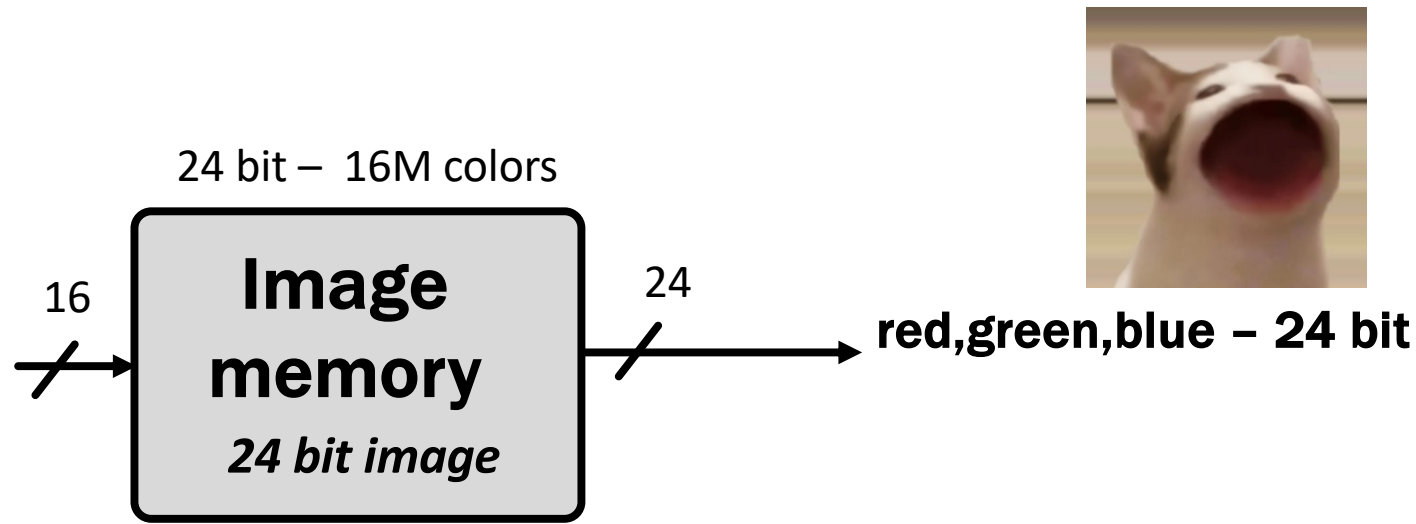- We could build a *24bit-wide* memory that has 256x256 (65,536) entries (deep) in it (one for each pixel)
- Math: $256 \times 256 \times 24 = 1,572,864$ bits
- That's greater than >50% of our memory on the S50 FPGA.




Strategy


- Images are large and take up lots of memory
- Want to save space, and store image using less memory
- Many images don't express every one of the 2^{24} "true" colors.
- Why waste the space storing an unused possibility?
- So pick the N most popular and only display them:
 - You can store them using $\text{ceil}(\log_2(N))$ bits (save space)
 - Then use a color table to look up what full color (24 bit value) that corresponds to!

Color Lookup Table

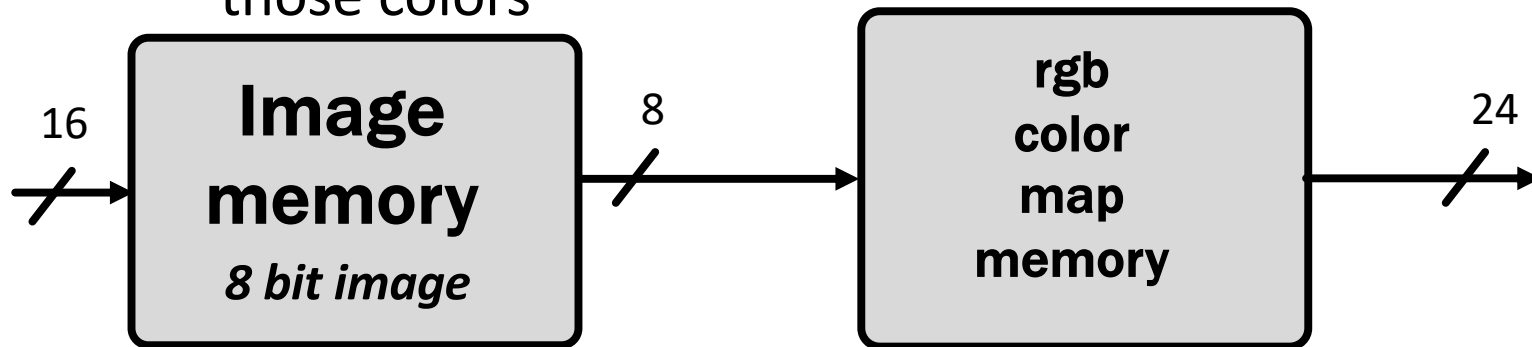- So use two memories:
 - 8-wide memory with 65536 entries for each pixel encoding one of 256 colors
 - 24-wide memory with 256 entries encoding those colors



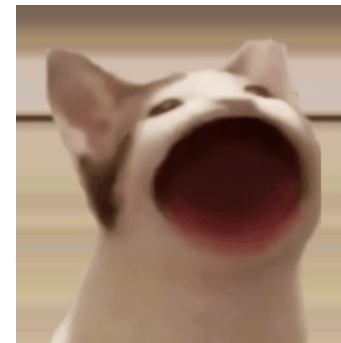Colors are still 24 bit, but the pixels are encoded using only 8 bits




**red,
green,
blue – 24 bit**

Storage Savings



24 bit – 16M colors

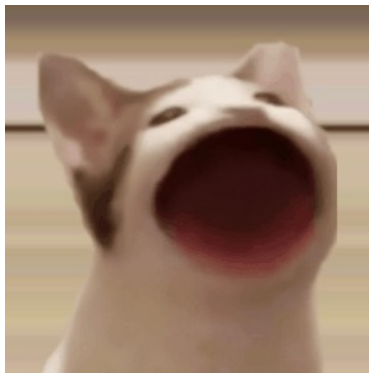256 X 256 image @ 24 bits per pixel is:
 $256 \times 256 \times 24 \text{ bits} = 1.572 \text{ Mbits}$
(196.6 kBytes)




8 bit – 256 colors

256 X 256 image with 8 bit color map:
 $256 \times 256 \times 8 \text{ bits} + 256 \times 24 = 0.530432 \text{ Mbits}$
(66.304 kBytes)


Keep Going As Needed



24 bit – 16M colors

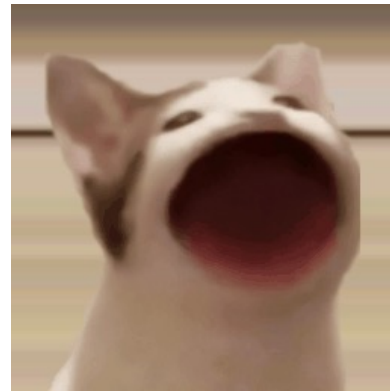

8 bit – 256 colors

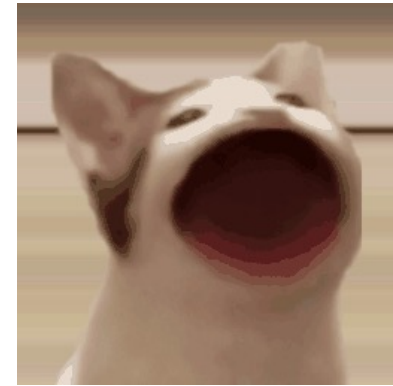

6 bit – 16 colors



4 bit – 16 colors



2 bit – 4 colors



1 bit – 2 colors

Additional Tricks Can be Played

- Dithering, in particular can help with this problem, but we'll go into that in a future week.


What about Latency?

- Yes What about latency.
- These things we just built are memories!
- Memory of any scale usually has latency involved with it
- Xilinx BRAM has how many cycles latency on a read?
- 2 cycles
- Lab/Week 5 will investigate

FSM Modularity


Toward FSM Modularity

- Consider the following abstract FSM:

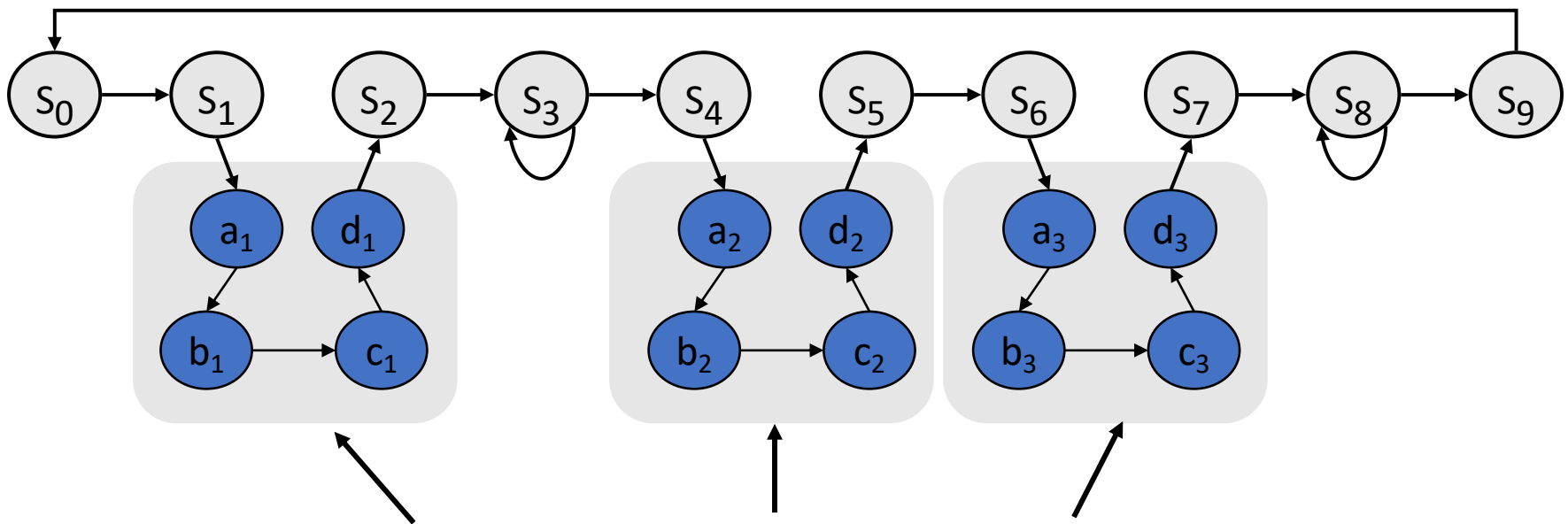


- Suppose that each set of states $a_x \dots d_x$ is a “sub-FSM” that produces exactly the same outputs.
- Can we simplify the FSM by removing equivalent states?
No! The outputs may be the same, but the next-state transitions are not.
- This situation closely resembles a **procedure call** or **function call** in software...how can we apply this concept to FSMs?

The Major/Minor FSM Abstraction

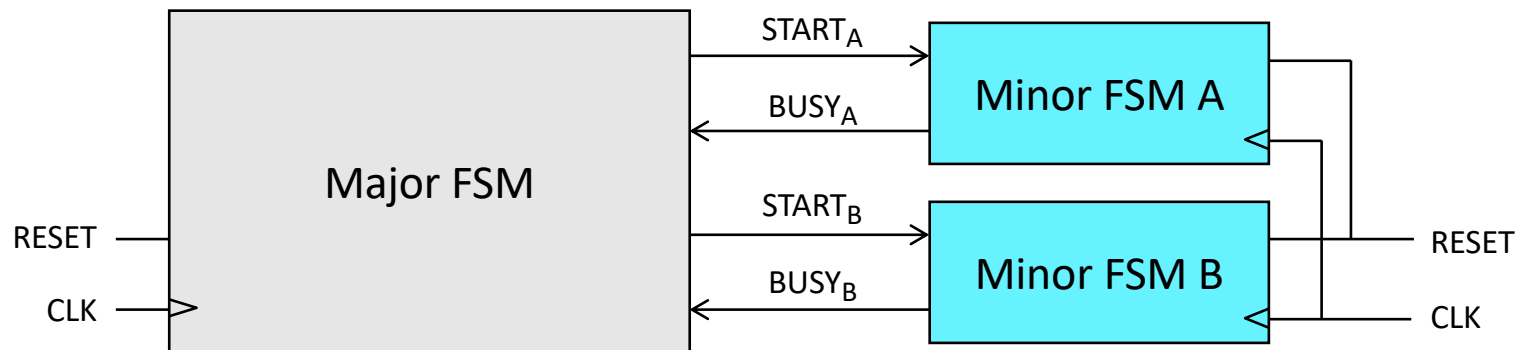

- Subtasks are encapsulated in **minor FSMs** with common reset and clock
- Simple communication abstraction:
 - START: tells the minor FSM to begin operation (the call)
 - BUSY: tells the major FSM whether the minor is done (the return)
- The major/minor abstraction is great for...
 - Modular designs (*always* a good thing)
 - Tasks that occur often but in different contexts
 - Tasks that require a variable/unknown period of time
 - Event-driven systems


Inside the Major FSM

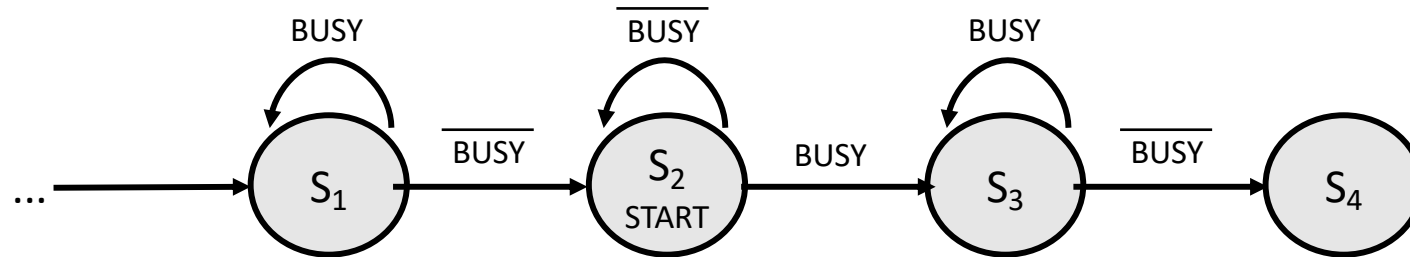

1. Wait until the minor FSM is ready

2. Trigger the minor FSM (and make sure it's started)



3. Wait until the minor FSM is done

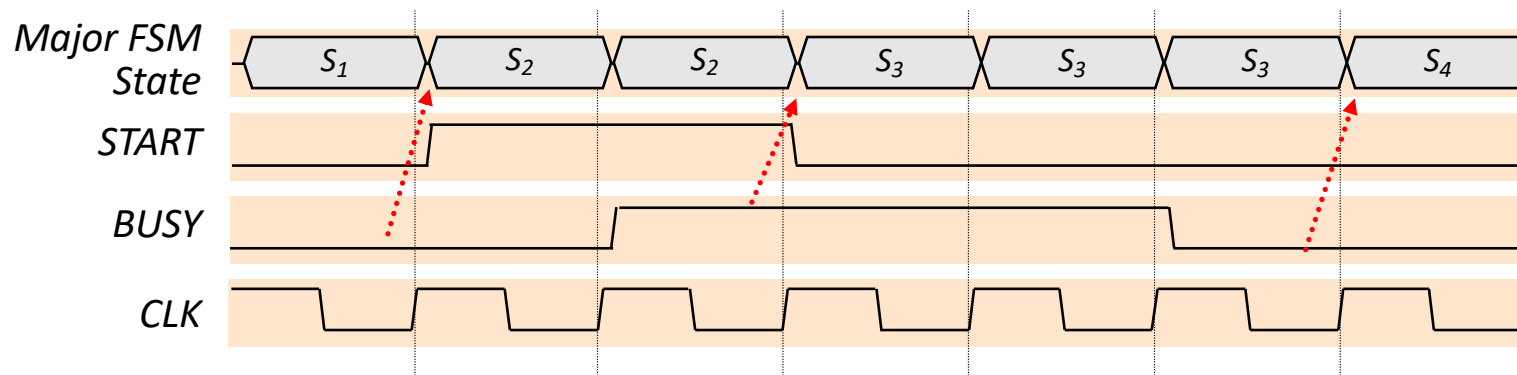

Variations:


- Usually don't need both Step 1 and Step 3
- One cycle "done" signal instead of multi-cycle "busy"

Inside the Minor FSM

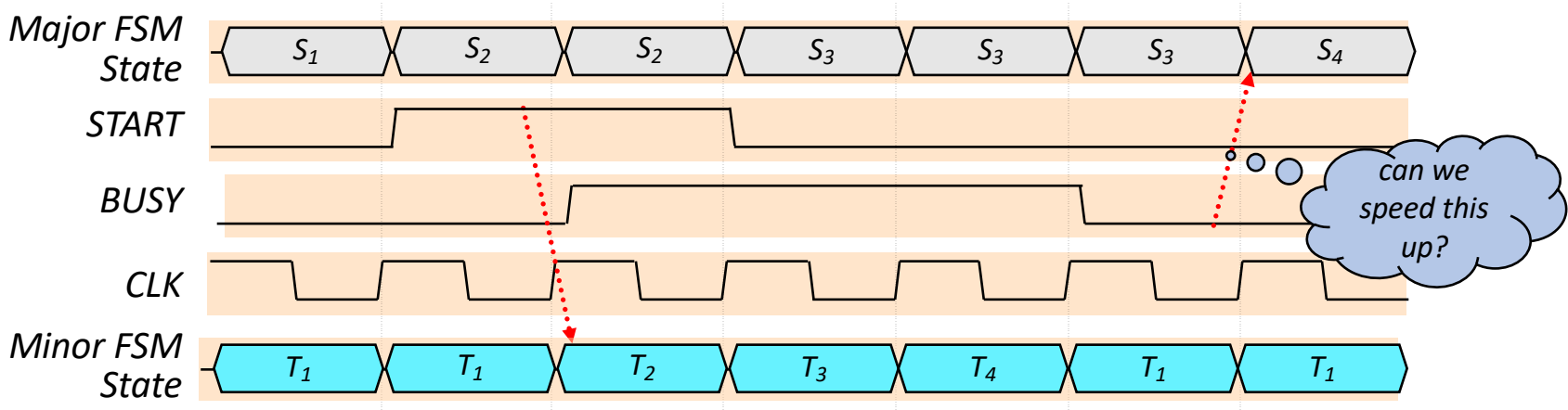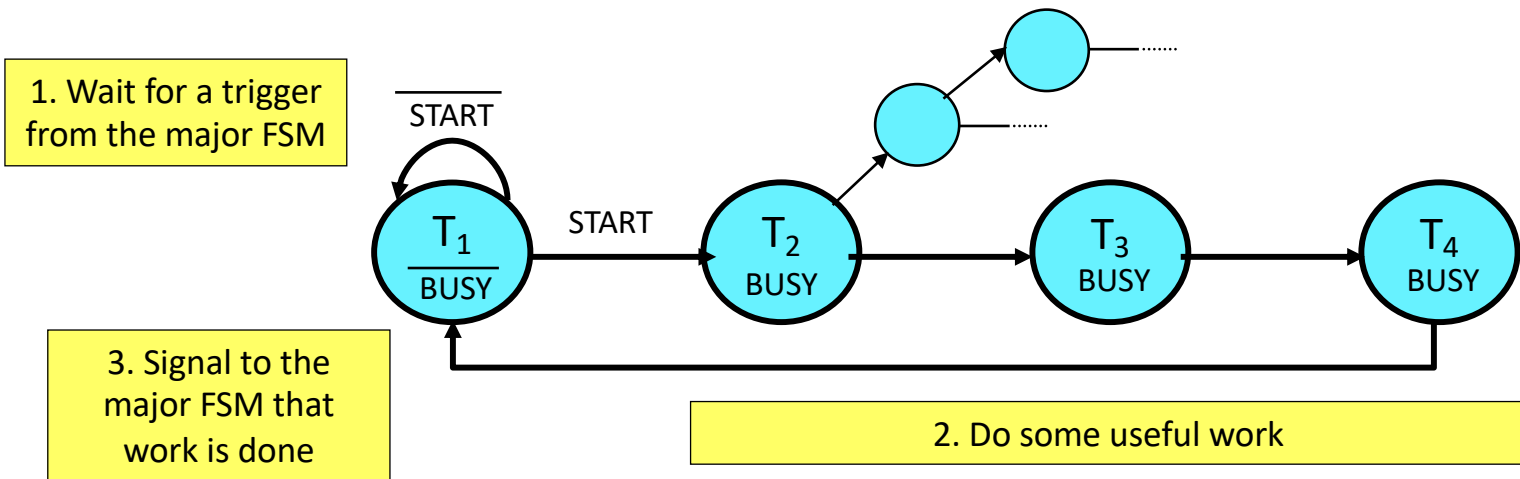


Optimizing the Minor FSM

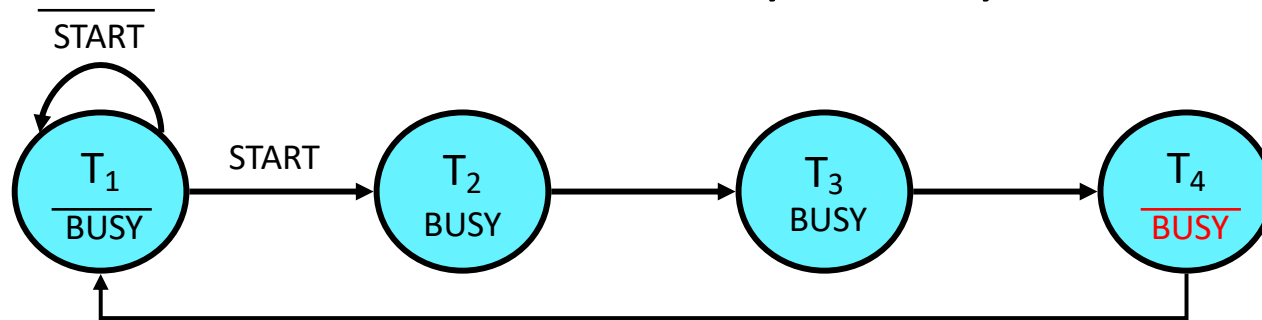Good idea: de-assert BUSY one cycle early




Bad idea #1:

T₄ may not immediately return to T₁

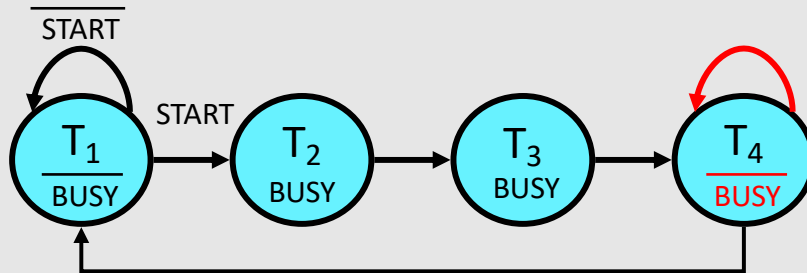


Bad idea #2:

BUSY never asserts!

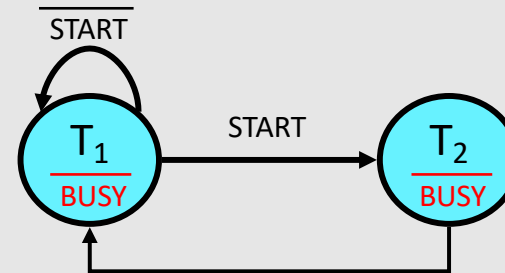


So make sure you if you do this, that last state always happens and always happens for one cycle

A Four-FSM Example


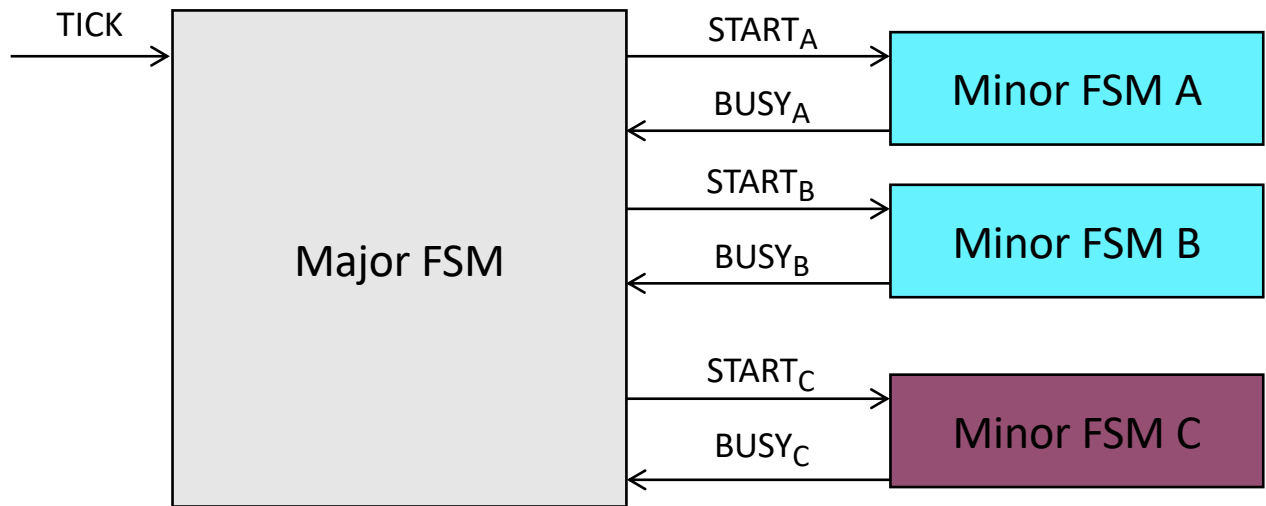


Operating Scenario:

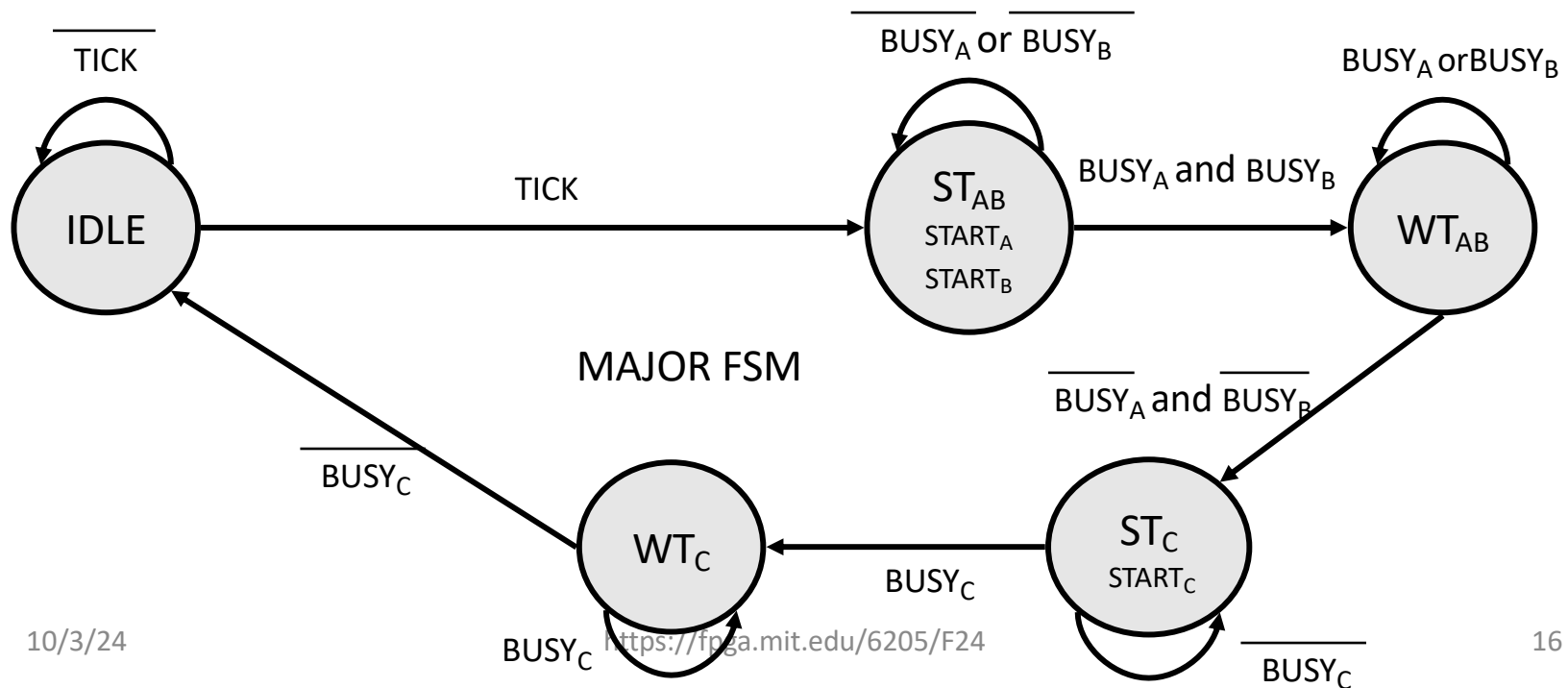- Major FSM is triggered by TICK
- Minors A and B are started simultaneously
- Minor C is started once both A and B complete
- TICKs arriving before the completion of C are ignored





Four-FSM Sample Waveform

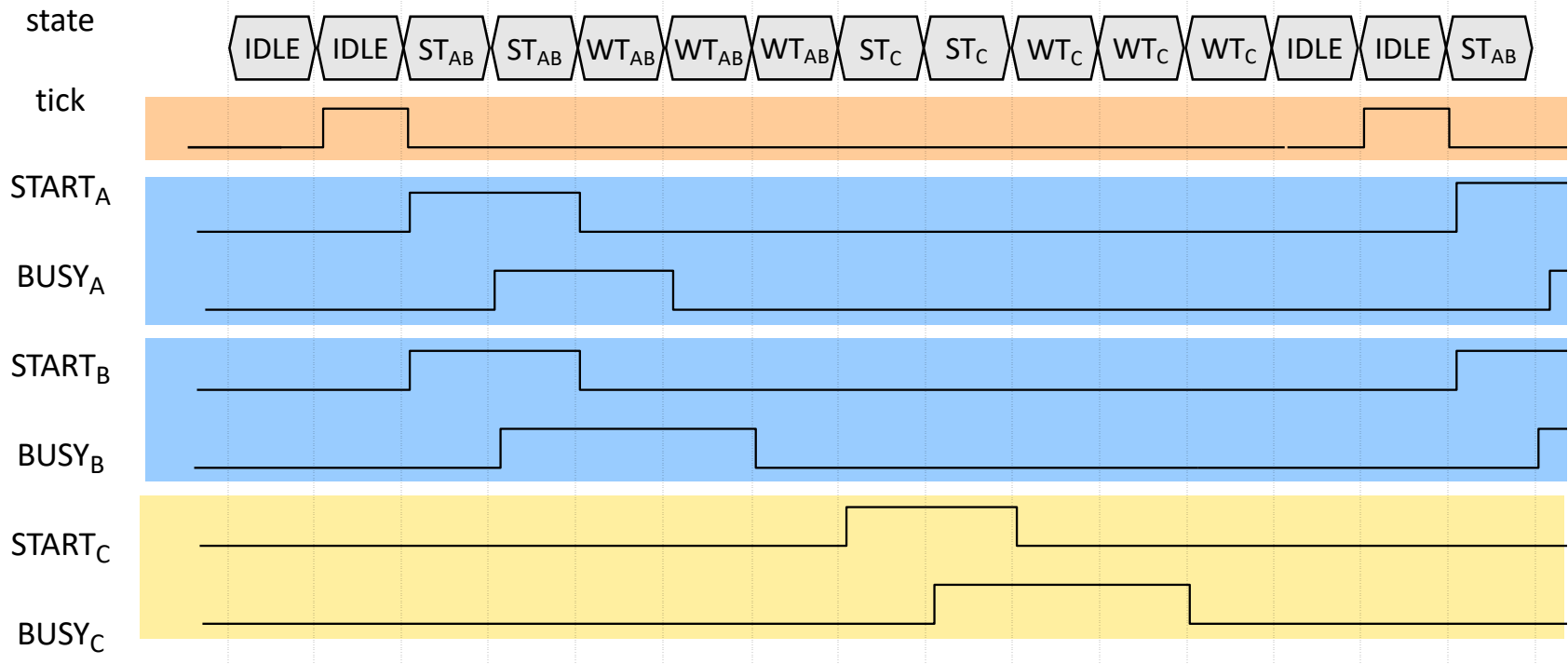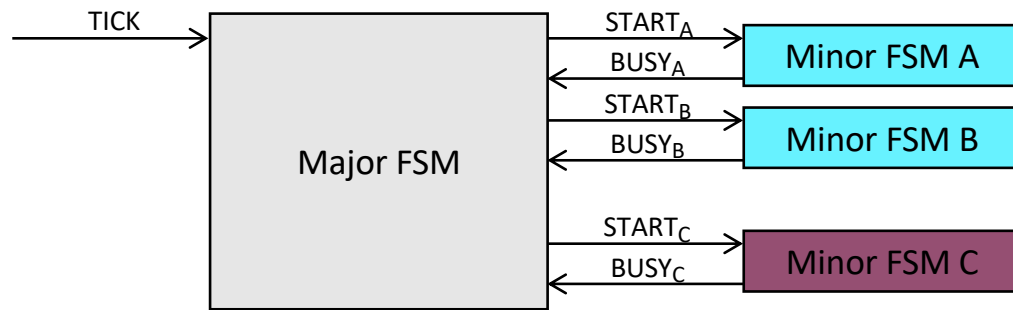

Alternative to Busy Signals

- As an alternative to busy signals sometimes just having a single-cycle “valid” signals is sufficient.
- If the downstream systems involved are stateful enough to be able to keep track of various system’s this can work
- Or you can do both. Depends on your design

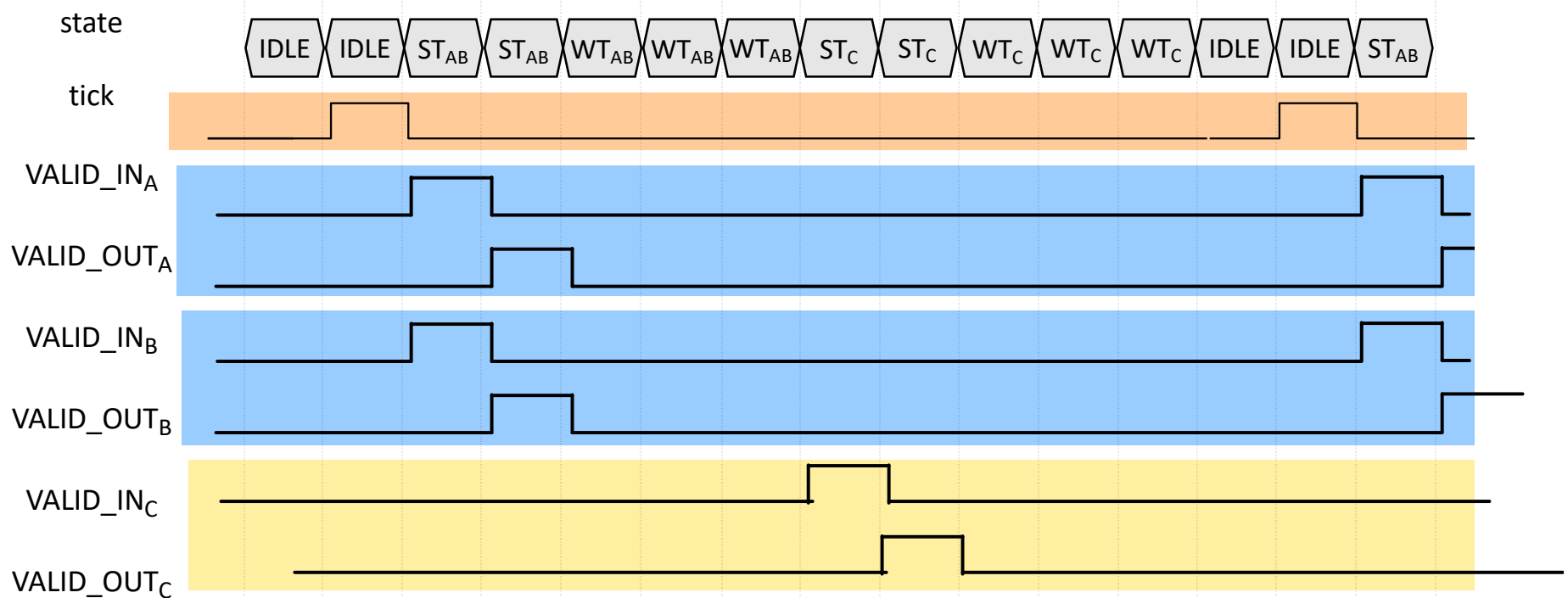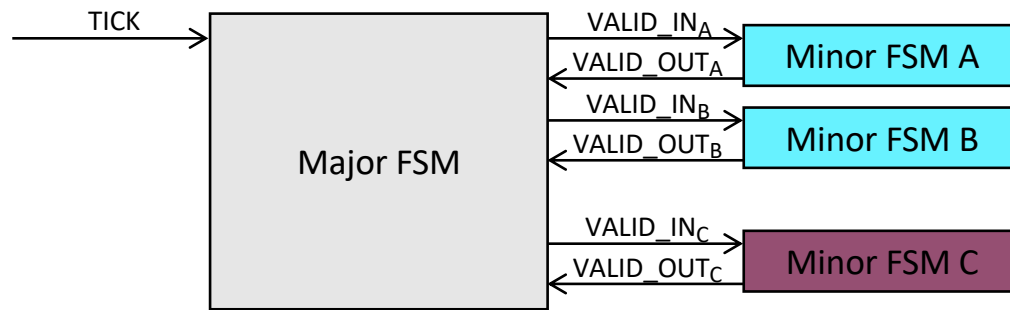Alternative to Busy Signals (Single-cycle asserts)



A Divider

- The Divider from when we first talked about FSMs is an example of a system which might be a minor FSM in part of a larger major's algorithm
- Many things need division, but it would suck to have to rewrite it repeatedly.
- We want you to get practice with that in Week 5's lab


```
module divider (input wire clk_in,
               input wire rst_in,
               input wire[15:0] dividend_in,
               input wire[15:0] divisor_in,
               input wire data_valid_in,
               output logic[15:0] quotient_out,
               output logic[15:0] remainder_out,
               output logic data_valid_out,
               output logic error_out,
               output logic busy_out);

localparam RESTING = 0;
localparam DIVIDING = 1;
logic [15:0] quotient, dividend, divisor;
logic state;
always_ff @(posedge clk_in)begin
  if (rst_in)begin
    quotient <= 16'b0;
    dividend <= 16'b0;
    divisor <= 16'b0;
    remainder_out <= 16'b0;
    busy_out <= 1'b0;
    error_out <= 1'b0;
    state <= RESTING;
    data_valid_out <= 1'b0;
  end else begin
    case (state)
      RESTING: begin
        if (data_valid_in)begin
          state <= DIVIDING;
          quotient <= 16'b0;
          dividend <= dividend_in;
          divisor <= divisor_in;
          busy_out <= 1'b1;
          error_out <= 1'b0;
        end
        data_valid_out <= 1'b0;
      end
      DIVIDING: begin
        if (dividend==0)begin
          state <= RESTING; //similar to return statement
          remainder_out <= divisor;
          quotient_out <= 0;
          busy_out <= 1'b0; //tell outside world i'm done
          error_out <= 1'b0;
          data_valid_out <= 1'b1; //good stuff!
        end else if (divisor==0)begin
          state <= RESTING;
          remainder_out <= 0;
          quotient_out <= 0;
          busy_out <= 1'b0; //tell outside world i'm done
          error_out <= 1'b1; //ERROR
          data_valid_out <= 1'b1; //valid ERROR
        end else if (dividend < divisor) begin
          state <= RESTING;
          remainder_out <= dividend;
          quotient_out <= quotient;
          busy_out <= 1'b0;
          error_out <= 1'b0;
          data_valid_out <= 1'b1; //good stuff!
        end else begin
          //state staying in.
          quotient <= quotient + 1'b1;
          dividend <= dividend-divisor;
        end
      end
    endcase
  end
end
endmodule
```

Center of Mass Calculation in Lab05

- You will write a center-of-mass calculator that is best thought of as an FSM.
- For each frame of video:
 - Sum the x location and y location of every active pixel you come across
 - Keep track of how many pixels you've encountered
 - At end of frame (or beginning of next one, divide the two sums by the number of active pixels
 - This will give an average X,Y
- Division takes time!
- Need to create a major/minor FSM system

Lab 05 Center of Mass

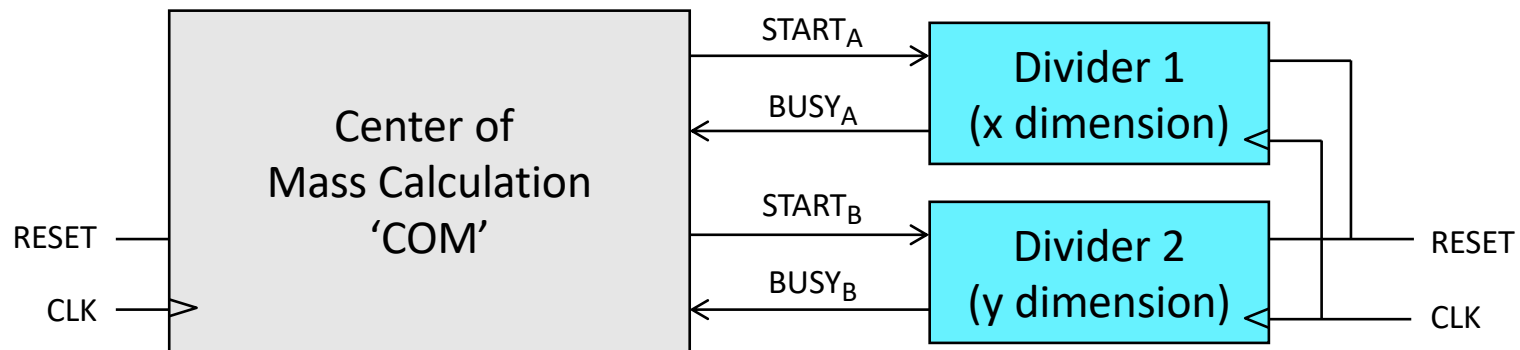


- C.O.M. will be in a “data collection state” during the active portion of a video frame
- When the frame’s active part is done, it needs to calculate the average x,y position of the “hot” pixels it has observed.
- To divide, the C.O.M. module hands the values it needs divided off to two separate dividers.
- C.O.M. waits on them monitoring their BUSY signals
- They can do division separately (in parallel)
- When done, they report back to the C.O.M with their result
- C.O.M. reports to outside world its calculation

Pipelining

How to make sure signals are balanced going through a sequence of operations.


Performance Metrics

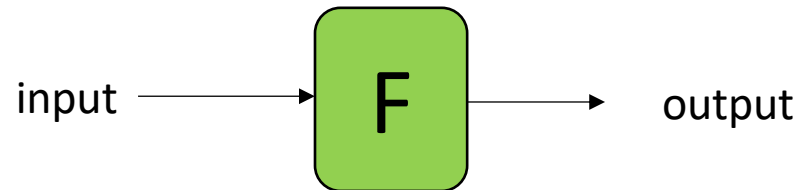

- Latency (L):
 - time between arrival of new input and generation of corresponding output.
 - For purely combinational circuits this is just t_{pD} .
- Throughput (T):
 - Rate at which new outputs appear.
 - For purely combinational circuits this is just $1/t_{pD}$ or $1/L$.


Performance of Combinational Logic

For combinational logic:

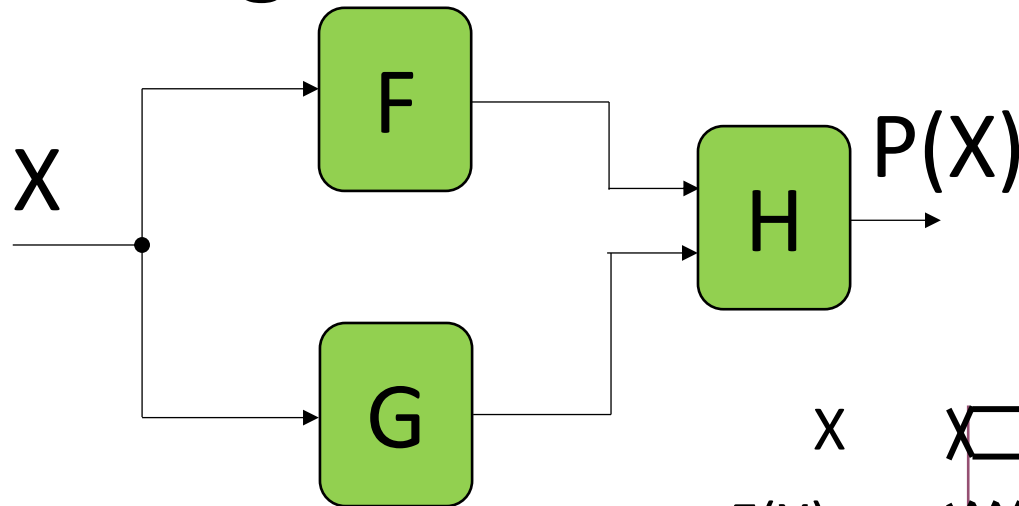

$$L = t_{PD},$$
$$T = 1/t_{PD}.$$

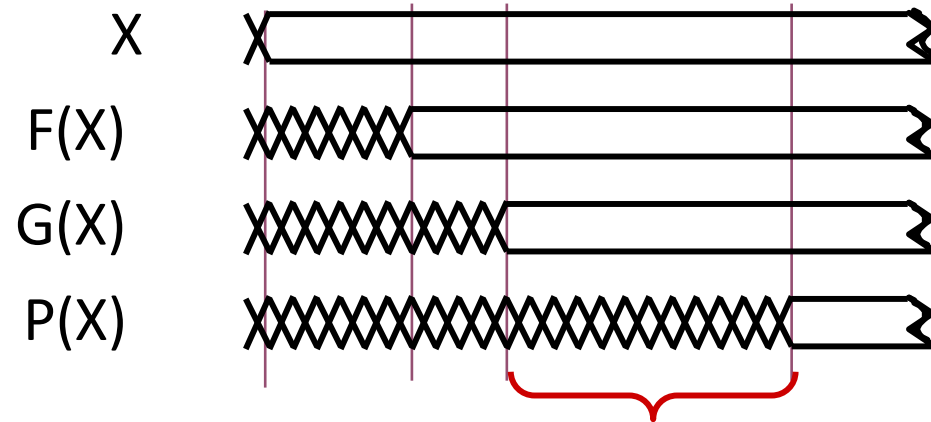
We can't get the answer faster, but are we making effective use of our hardware at all times?




F & G are "idle", just holding their outputs stable while H performs its computation

Retiming: A useful transform

Propagation delays indicated by numbers:

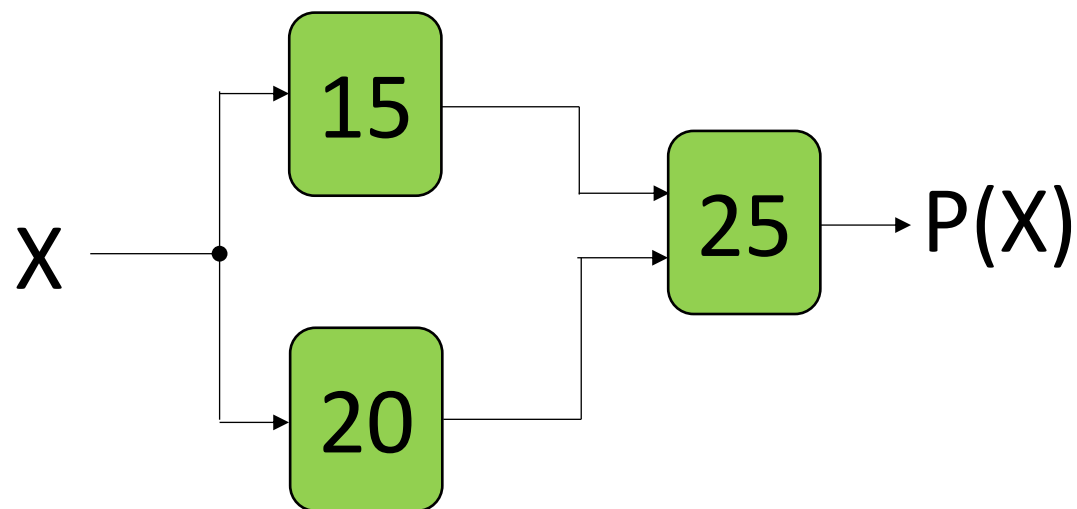


Retiming: A useful transform

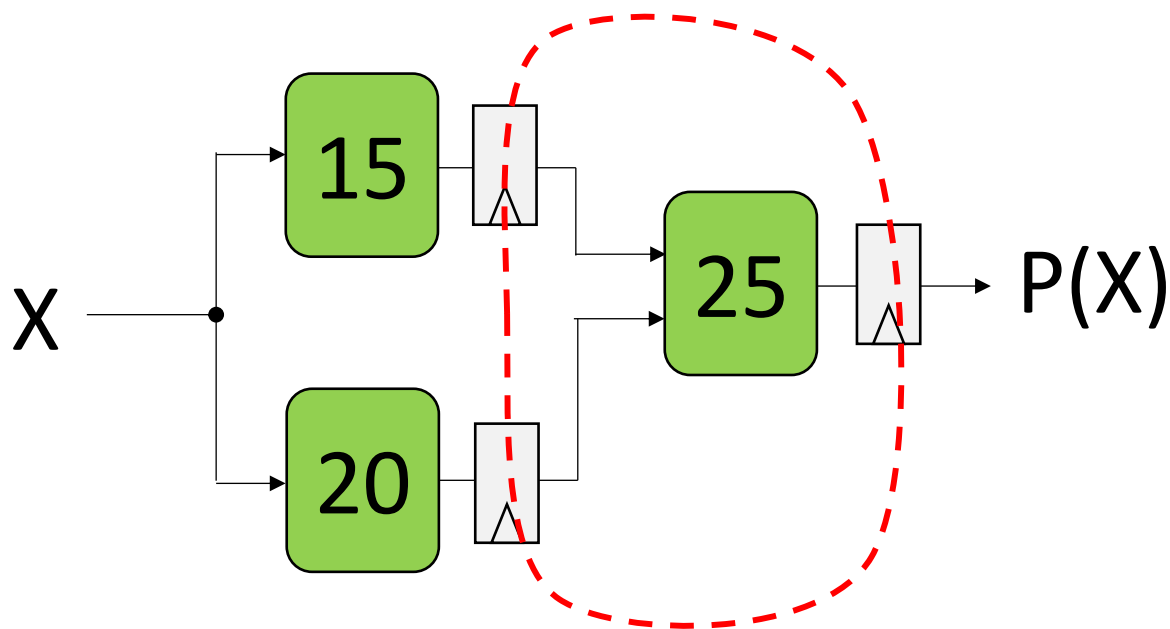

*Assuming ideal registers:
i.e., $t_{PD} = 0$, $t_{SETUP} = 0$*

Pipeline Diagrams

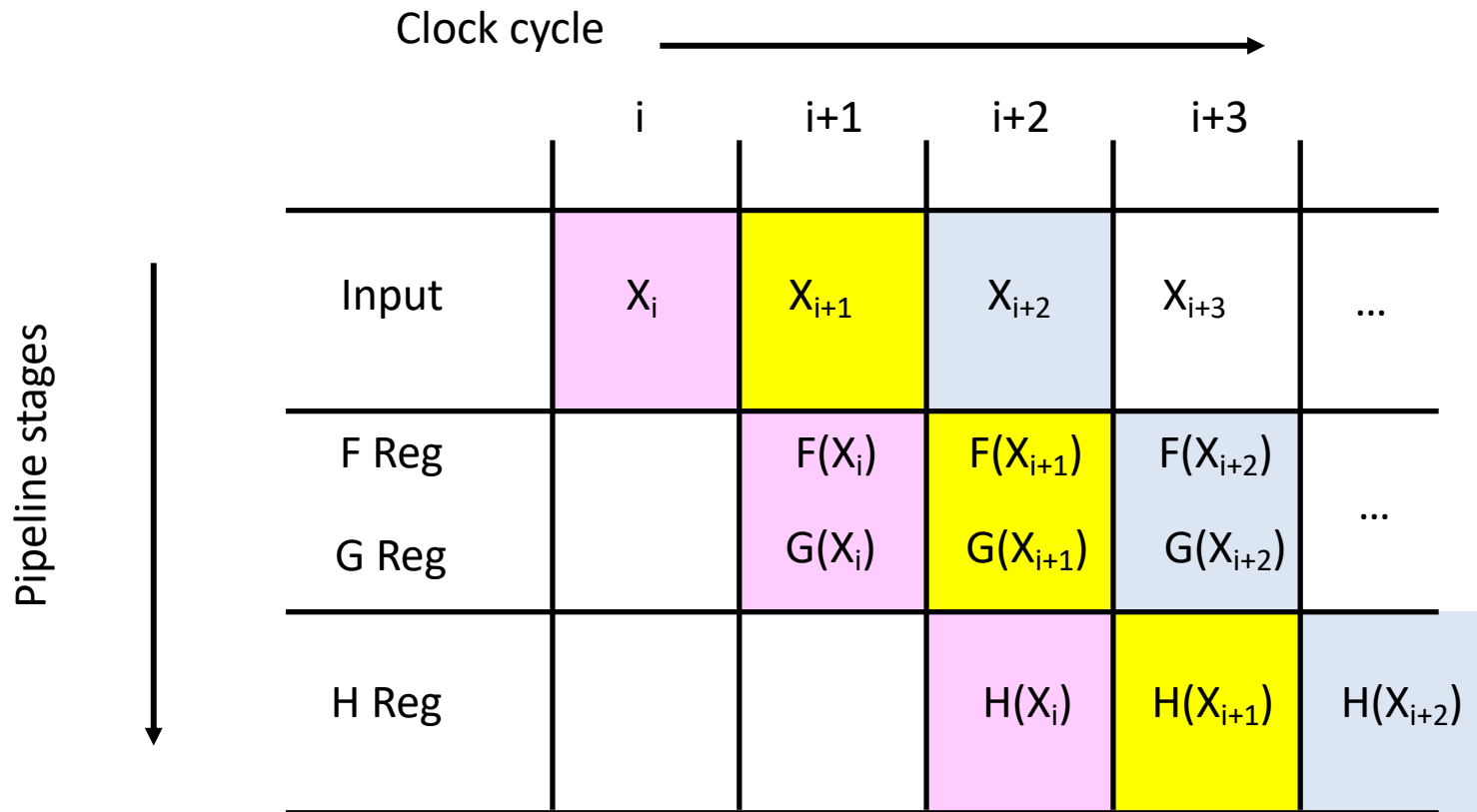

The results associated with a particular set of input data moves diagonally through the diagram, progressing through one pipeline stage each clock cycle.

Pipeline Conventions

- a **K-Stage Pipeline** (“K-pipeline”) is an acyclic circuit having exactly K registers on every path from an input to an output.
- a COMBINATIONAL CIRCUIT is thus a 0-stage pipeline.

Pipeline Conventions


- CONVENTION:
 - Every pipeline stage, hence every K-Stage pipeline, has a register on its OUTPUT (not on its input).
- ALWAYS:
 - The CLOCK common to all registers must have a period sufficient to cover propagation over combinational paths PLUS (input) register t_{PD} PLUS (output) register t_{SETUP} .

$$t_{PD,reg1} + t_{PD,logic} + t_{SETUP,reg2} \leq t_{CLK}$$

The LATENCY of a K-pipeline is K times the period of the clock common to all registers.

The THROUGHPUT of a K-pipeline is the frequency of the clock.

ILL-formed Pipeline

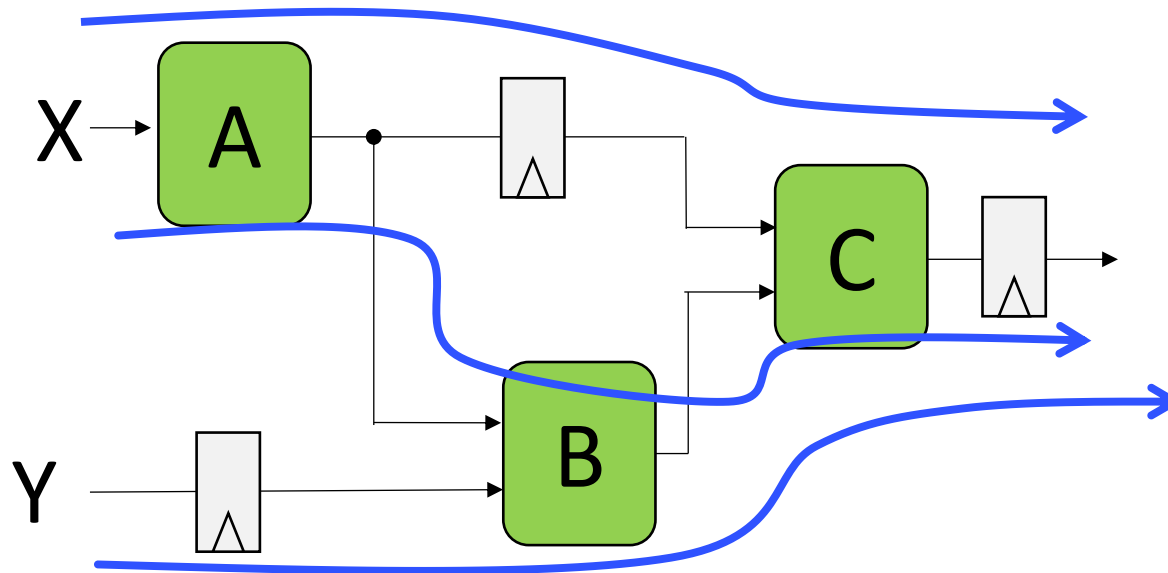

For what value of K is the following circuit a K-Pipeline? none


Problem:

Successive inputs get mixed: e.g., $B(A(X_{i+1}), Y_i)$. This happened because some paths from inputs to outputs have 2 registers, and some have only 1!

This CAN'T HAPPEN on a well-formed K pipeline!


Pipelining

Let's say we want t_{clk} to be 8ns

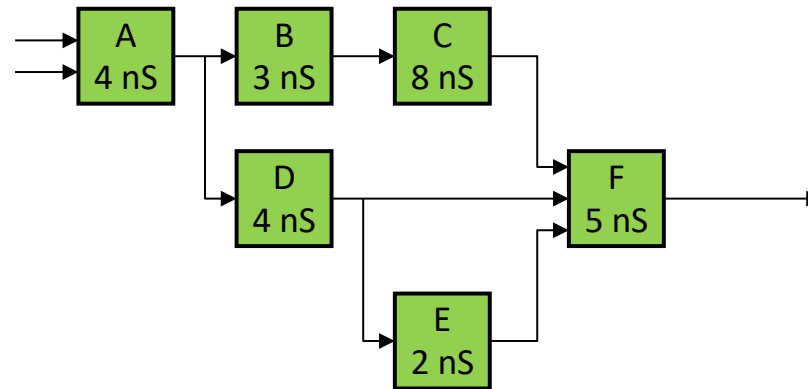

Another Thing to Pipeline

Let's say we want t_{clk} to be 8ns

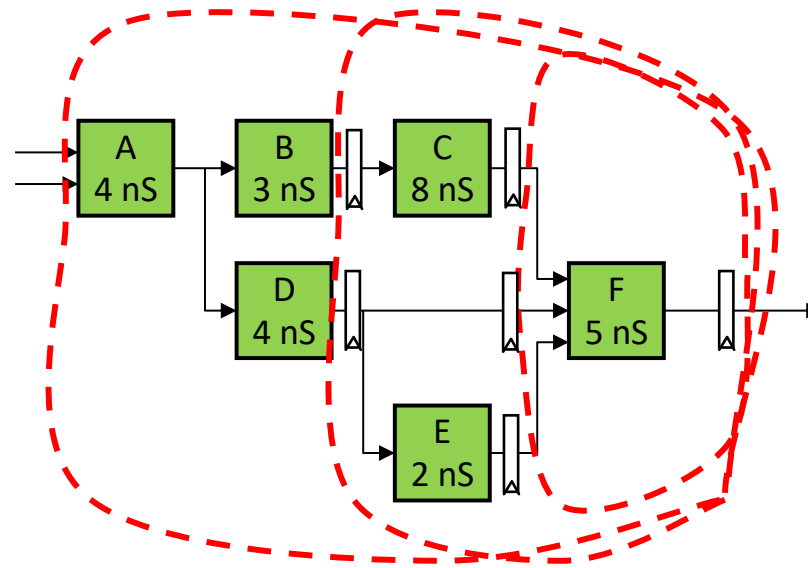

Step 1:

Add a register on the output.


Step 2:

From register. Draw a contour backwards that includes as much of the circuit that will fit inside required period. Add registers

Repeat until satisfied with T. Look for redundant registers


STRATEGY:

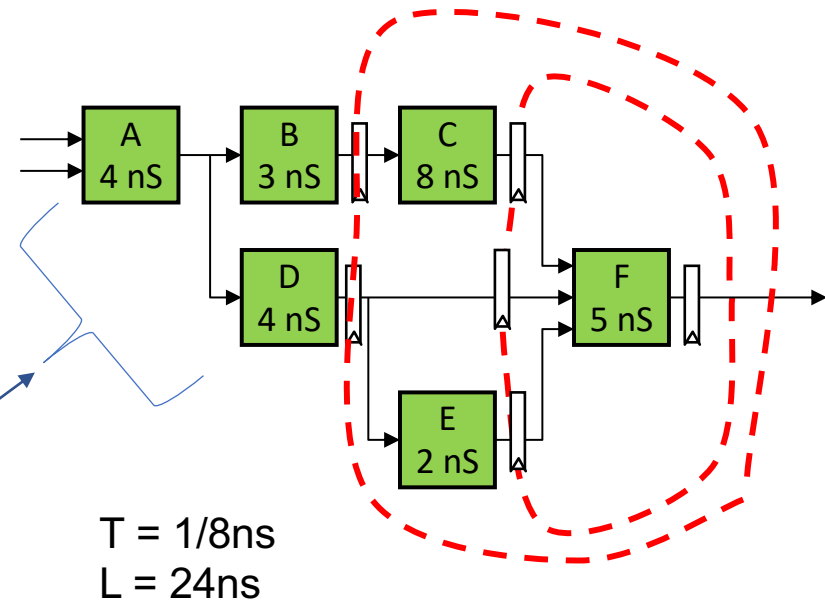Focus your attention on placing pipelining registers around the slowest circuit elements (BOTTLENECKS).



Assuming this interfaces with other modules that have registered outputs the input will chain will be ok ($\leq 8ns$)

Another Pipeline Example

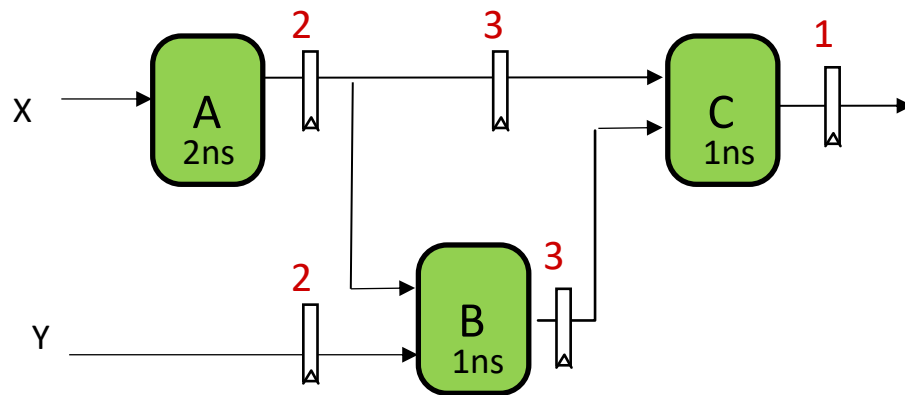


OBSERVATIONS:

- 1-pipeline improves neither L or T.
- T improved by breaking long combinational paths, allowing faster clock.
- Too many stages cost L, don't improve T.
- Back-to-back registers are often required to keep pipeline well-formed.


| | LATENCY | THROUGHPUT |
|---------|---------|------------|
| 0-pipe: | 4ns | 1/4ns |
| 1-pipe: | 4ns | 1/4ns |
| 2-pipe: | 4ns | 1/2ns |
| 3-pipe: | 6ns | 1/2ns |

Better throughput here means we can run at higher clock rate

Pipelining in Verilog

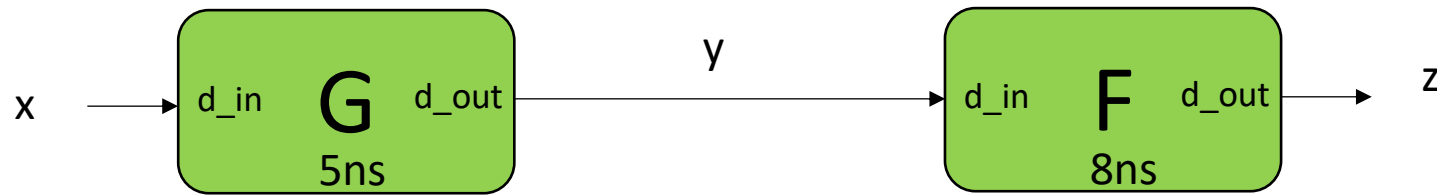
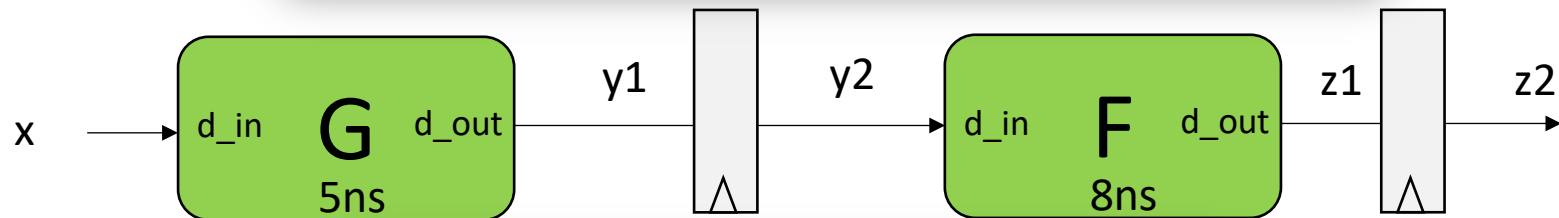
```
1
2 logic x,y,z;
3 //G and F are purely combinational modules.
4 G myg (.d_in(x), .d_out(y));
5 F myf (.d_in(y), .d_out(z));
```



```
1
2 logic x,y1,y2,z1,z2;
3 //G and F are purely combinational modules.
4 G myg (.d_in(x), .d_out(y1));
5 F myf (.d_in(y2), .d_out(z1));
6
7 always_ff @(posedge clk)begin
8   y2 <= y1;
9   z2 <= z1;
10 end
11
```

How often should you be adding FlipFlops in your FPGA?

- This comes with experience and getting to know your system.
- Most of what you want to do really is some form of math.
- So knowing how much math you can do in a clock cycle is useful


The Complexity of Math Operations

Let's look at some basic math circuits:


$+$, $-$, $*$, $/$

“Full Adder” building block

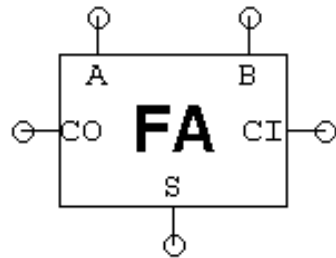The “half adder” circuit has only the A and B inputs (no carry)
Full adders handle carry bits



| A | B | CI | S | CO |
|---|---|----|---|----|
| 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 1 | 0 |
| 0 | 1 | 0 | 1 | 0 |
| 0 | 1 | 1 | 0 | 1 |
| 1 | 0 | 0 | 1 | 0 |
| 1 | 0 | 1 | 0 | 1 |
| 1 | 1 | 0 | 0 | 1 |
| 1 | 1 | 1 | 1 | 1 |

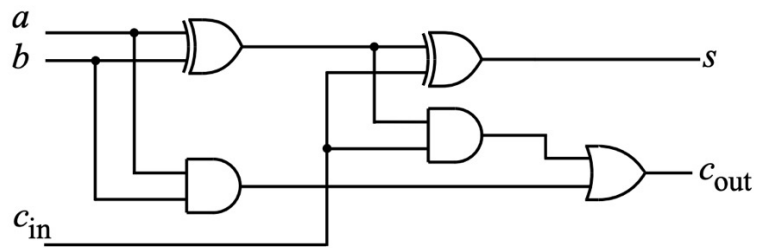

Adder: a circuit that does addition


Here's an example of binary addition as one might do it by "hand":

Adding two N-bit numbers produces an (N+1)-bit result


$$\begin{array}{r} 1101 \\ + 0101 \\ \hline 10010 \end{array}$$

Carries from previous column

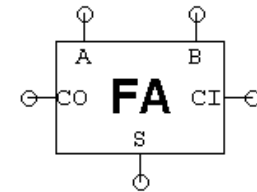If we build a circuit that implements one column:



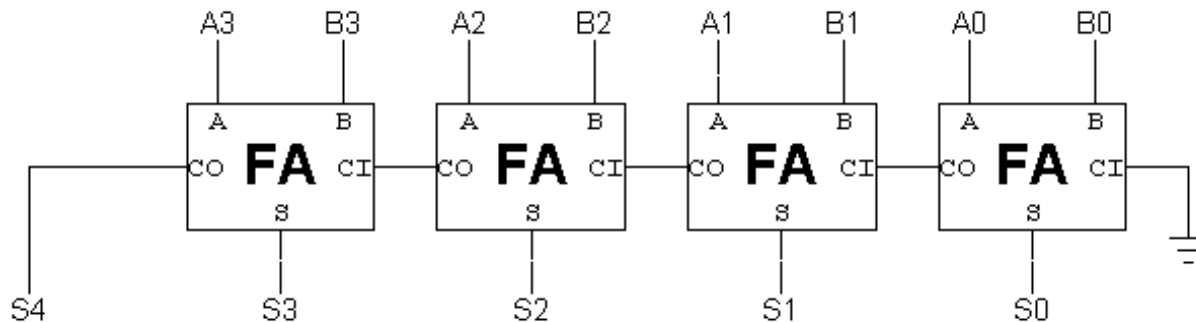we can quickly build a circuit to add two 4-bit numbers...



"Ripple-carry adder"


Subtraction: $A - B = A + (-B)$

Using 2's complement representation: $-B = \sim B + 1$

\sim = bit-wise complement



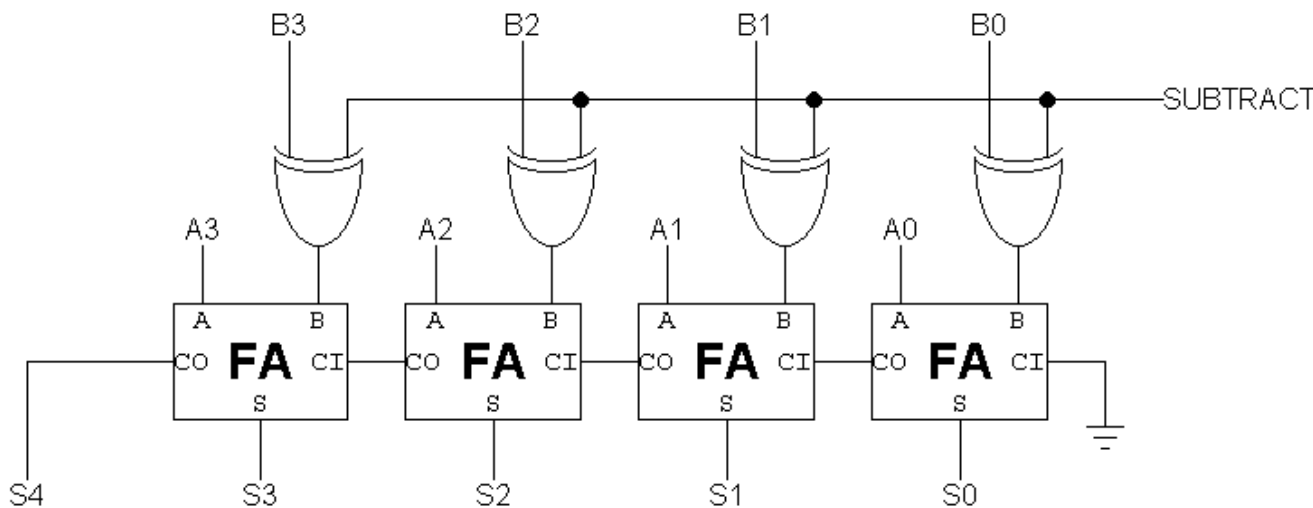So let's build an arithmetic unit that does both addition and subtraction.
Operation selected by control input:




When *SUBTRACT* is 1:


- Invert each bit
- Start with a Carry of 1 (same as adding 1)

“Full Adder” building block

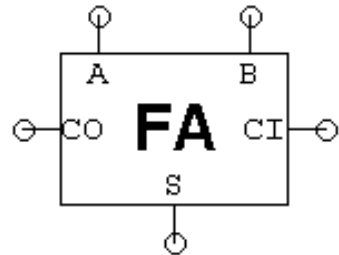The “half adder” circuit has only the A and B inputs



| A | B | CI | S | CO |
|---|---|----|---|----|
| 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 1 | 0 |
| 0 | 1 | 0 | 1 | 0 |
| 0 | 1 | 1 | 0 | 1 |
| 1 | 0 | 0 | 1 | 0 |
| 1 | 0 | 1 | 0 | 1 |
| 1 | 1 | 0 | 0 | 1 |
| 1 | 1 | 1 | 1 | 1 |

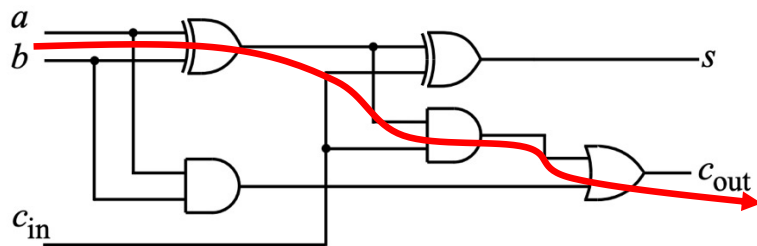


t_{pd} dictated by carry path!

Can also rewrite the carry path as: $c_{out} = (a \& c_{in}) \vee (b \& c_{in}) \vee (a \& b)$

Speed: t_{PD} of Ripple-carry Adder

$$C_O = AB + AC_I + BC_I$$

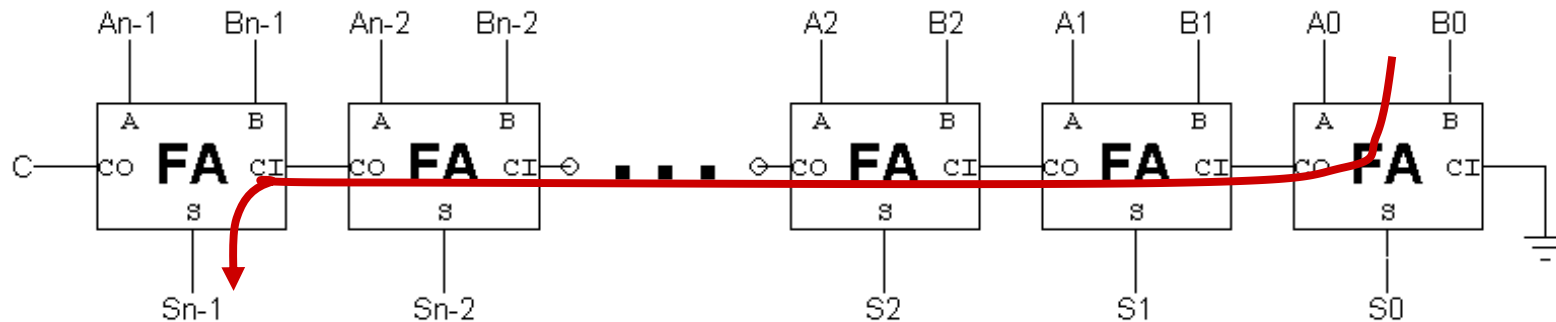

Worst-case path: carry propagation from LSB to MSB, e.g., when adding 11...111 to 00...001.

$$t_{PD} = \underbrace{(N-1) * (t_{PD,OR} + t_{PD,AND})}_{CI \text{ to } CO} + \underbrace{t_{PD,XOR}}_{CI_{N-1} \text{ to } S_{N-1}} \approx \Theta(N)$$

$\Theta(N)$ is read “order N”: means that the latency of our adder grows at worst in proportion to the number of bits in the operands.

$$t_{adder} = (N-1)t_{carry} + t_{sum}$$


The Carry Path Becomes Limiting

- Solution is the Carry-Look-ahead Adder:

$$\begin{aligned}c_1 &= G_0 + P_0.c_0 \\c_2 &= G_1 + P_1.G_0 + P_1.P_0.c_0 \\c_3 &= G_2 + P_2.G_1 + P_2.P_1.G_0 + P_2.P_1.P_0.c_0 \\c_4 &= G_3 + P_3.G_2 + P_3.P_2.G_1 + P_3.P_2.P_1.G_0 + P_3.P_2.P_1.P_0.c_0\end{aligned}$$

Can do some factoring/redesign and cut-down on t_{pd} of the carry path
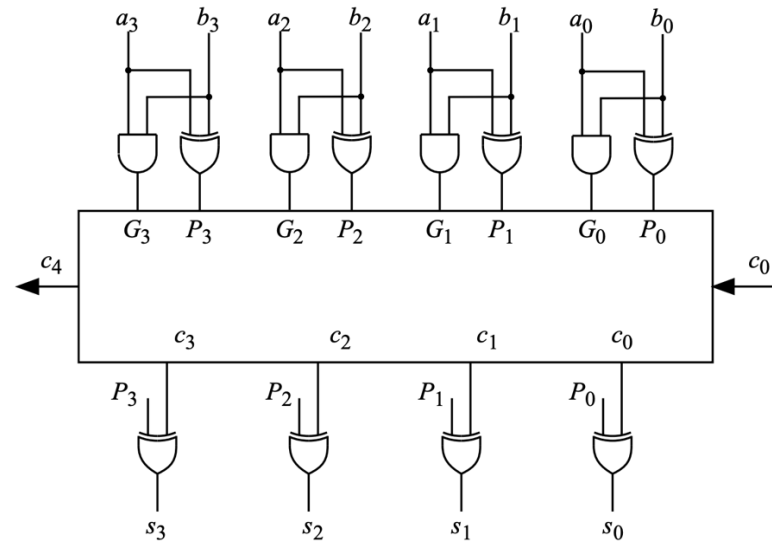
$$\begin{aligned}G_i &= a_i.b_i \\P_i &= a_i \oplus b_i\end{aligned}$$




https://www.ece.uvic.ca/~fayez/courses/ceng465/lab_465/project1/adders.pdf

Logic Slices Can Add/Subtract

- Can synthesize the addition of two 4 bit numbers with fast carry
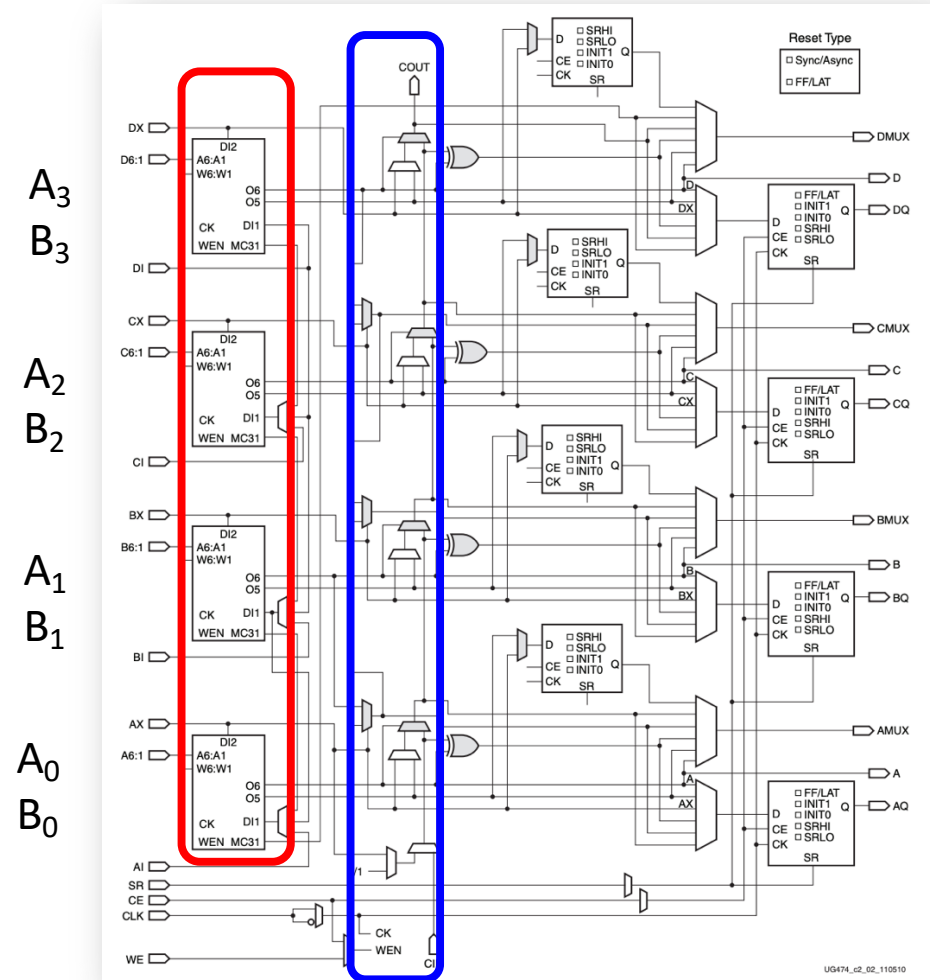
$$\begin{array}{r} A_3A_2A_1A_0 \\ + B_3B_2B_1B_0 \\ \hline \end{array}$$



Fast Carry-Chain


Series 7 Logic Slice

Add/Subtract on the FPGA

- + and – can be done combinatorially very quickly:
 - 32 bit add can be done in a clock cycle (<10 ns) pretty easily
 - Several smaller adds (A+B+C+D) can be done in clock cycle as well (10 ns)
- CLBs (the generic function generators, of which we have a lot) are capable of being chained together to allow large adds.

Slices can stack to give more bits
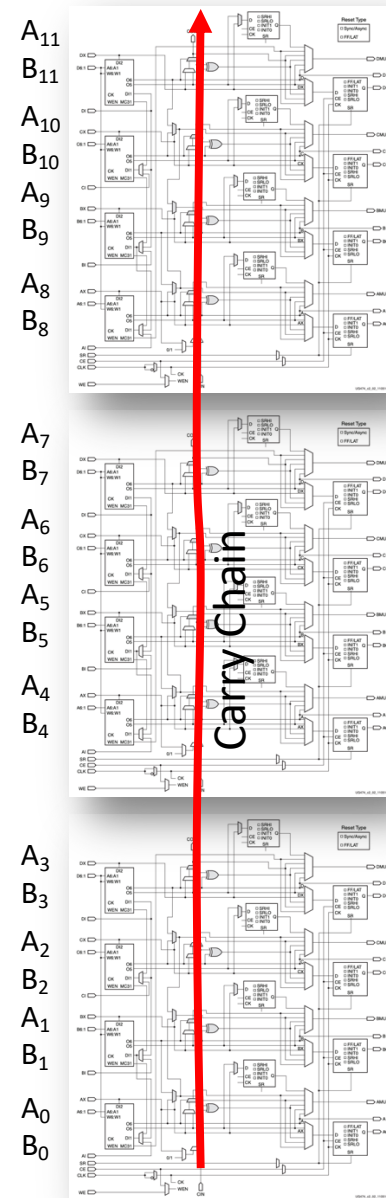
$$\begin{array}{r} A_{11}A_{10}A_9A_8A_7A_6A_5A_4A_3A_2A_1A_0 \\ + B_{11}B_{10}B_9B_8B_7B_6B_5B_4B_3B_2B_1B_0 \end{array}$$



+ or - in Verilog

- Generally + or – on its own will get synthesized using logic slices unless specified
- Very large additions or subtractions may start to take too long!*
- But doing a couple 32 bit adds in a 10 ns cycle should be possible...

**too is really with respect to a clock. If you're running on a 10 MHz clock, then things are different!*

But also the stuff around it matters too!

- Keep track of the stuff before and after your math.
- If you have a ton of if/else/ifs...or if you have a super-deeply nested if/if/if/ chain, all that stuff requires logic too.

Also Case Statements are Good

- If/elses and even parallel if's as shown on the previous page get encoded as priority logic

```
always_ff @(posedge clk)begin
  if (state == IDLE) begin
    q <= y;
  end else if (state == FIRST) begin
    q <= z;
  end else if (state == SECOND) begin
    q <= zzz;
  end else begin
    q <= zzz;
  end
end
```

long combinational path

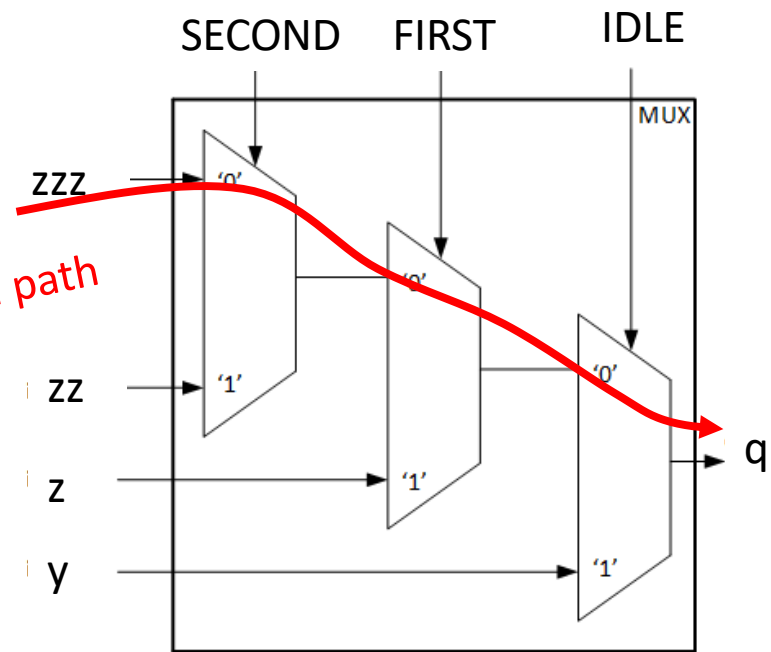



Fig 1

Also Case Statements are Good

- If logic can be structured without priority, then do it! Can yield simpler underlying logic.

```
always_ff @(posedge clk)begin
  case(state)
    IDLE: begin
      q <= y;
    end
    FIRST: begin
      q <= z;
    end
    SECOND: begin
      q <= zz;
    end
    default: begin
      q <= zzz;
    end
  endcase
end
```

shorter combinational path

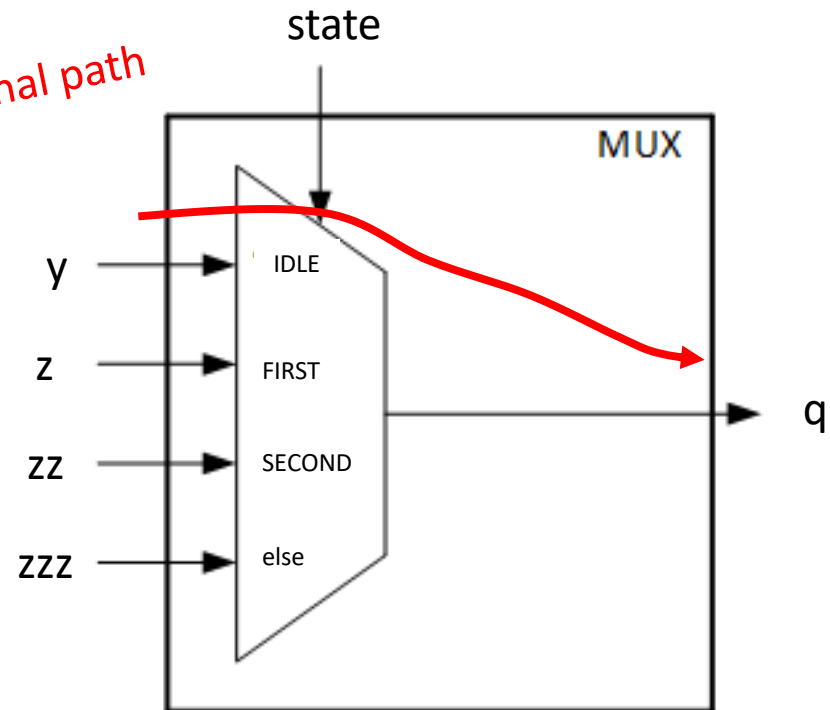

https://www.kevnugent.com/2020/10/22/verilog-blogpost_002/

The stuff around it matters too!

- Keep track of the stuff before and after your math.
- If you have a ton of if/else/ifs...or if you have a super-deeply nested if/if/if/ chain, all that stuff requires logic too.
- **Also think about the stuff being used to calculate the if/else stuff.**

Example...

I violate timing!

```
logic [31:0] a,b,y,z,q,s,t,r;  
always_ff @(posedge clk)begin  
  if (b > q;)begin  
    a <= y+z;  
  end  
end
```

```
always_comb begin  
  q = s + t;  
end
```

```
always_comb begin  
  t = r>98?r+100:a+11;  
end
```

Path that needs to be calculated

Multiplication on the FPGA

- Multiplication can be done on the FPGA on 2's complement numbers
- Takes more time:
 - Depending on size of operands may/may not be doable in one clock cycle
- Where possible try to get away with bit shifts and adds.

Multiplications with shifts

- $\ll 1$ is multiply by 2
- $\gg 1$ is divide by 2
- Can do a lot with this if get creative

```
1
2  logic [7:0] x;
3  logic [7:0] y; //want this to be seven times X
4  assign y = (x<<2) + (x<<1) + x;
5
```

- Vivado can be pretty good at figuring these things out for you, but largely only for constants.

Generic Digital Multiplication

$$\begin{array}{r}
 \begin{array}{cccc}
 a_3 & a_2 & a_1 & a_0 \leftarrow \text{Multiplicand} \\
 b_3 & b_2 & b_1 & b_0 \leftarrow \text{Multiplier}
 \end{array} \\
 \hline
 \begin{array}{r}
 X \\
 \begin{array}{cccc}
 a_3b_0 & a_2b_0 & a_1b_0 & a_0b_0 \\
 a_3b_1 & a_2b_1 & a_1b_1 & a_0b_1 \\
 a_3b_2 & a_2b_2 & a_1b_2 & a_0b_2 \\
 a_3b_3 & a_2b_3 & a_1b_3 & a_0b_3
 \end{array}
 \end{array}
 \left. \vphantom{\begin{array}{r} X \\ \dots \end{array}} \right\} \text{Partial products} \\
 \hline
 \dots \quad a_1b_0 + a_0b_1 \quad a_0b_0 \leftarrow \text{Product}
 \end{array}$$

In base 2 multiplication these are all very simple calculations done with XOR

*Some really cool factoring can be done to make the overall propagation delay of a multiplier relatively short, though there's a lot of logic in it**

*Lecture on Multiplier architectures: <https://inst.eecs.berkeley.edu/~eecs151/sp18/files/Lecture21.pdf>

DSP Blocks

- Add-then-multiply is a common operation chain in many things, particularly Digital Signal Processing
- FPGA has dedicated hardware multiplier modules called DSP48 blocks on it
 - 150 of them on Urbana FPGA
 - Capable of single-cycle multiplies
- Can get inferred from using `*` in your Verilog that isn't a power of 2:
 - $x*y$, for example, will likely will result in DSP getting used
 - May take a full clock cycle so would need to budget timing accordingly
- Can infer multiple for larger multiplies

DSP48 Slice (High Level)

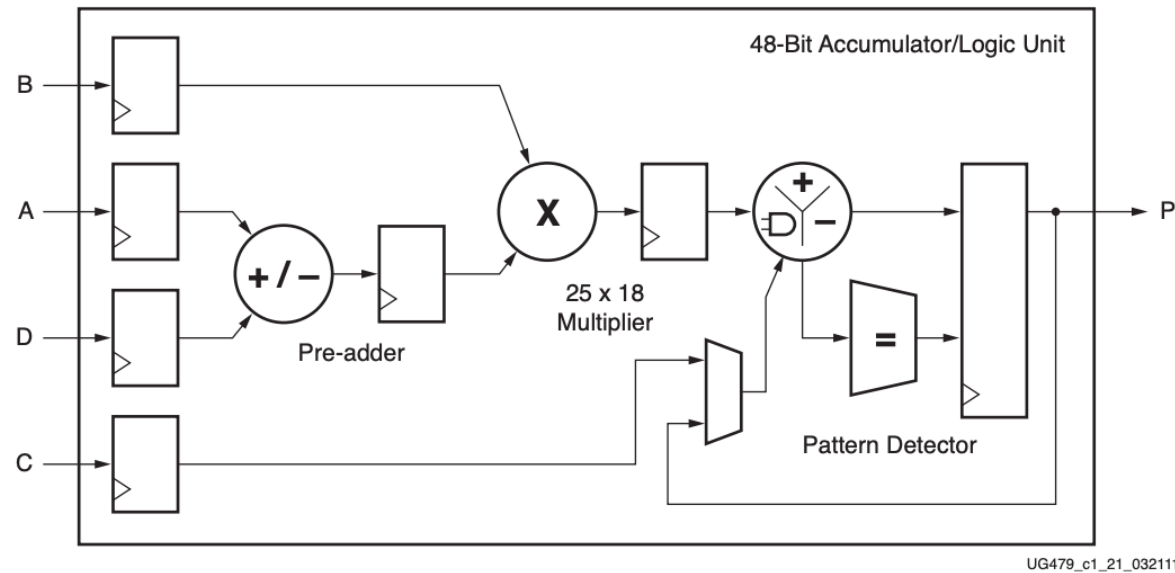


Figure 1-1: **Basic DSP48E1 Slice Functionality**

Much of the benefit/speed of this module comes from the hardwired internal routing, keeping it very fast. This device is not as generalized as a LUT/logic cell. It can only do a subset of math operations

https://www.xilinx.com/support/documentation/user_guides/ug479_7Series_DSP48E1.pdf

How much multiply can do?


- At 100 MHz on these boards, I'd aim for one 32 bit multiply per clock cycle (it'll use several DSP blocks to achieve that)
- Anything more is pushing it
- If you run out of DSP blocks, it'll revert to using the generic logic...and this will become a harder problem to satisfy
- Smaller multiply-adds you can maybe get away with in one clock cycle.

Division

- The outlier in the + - * / set...
- Division is a significantly harder math operation to do compared to multiplication
- Where possible try to avoid
- Try to divide by powers of 2 (use right shift)!

- If you can't avoid we must do it. (week 05)

Lab 05 Center of Mass

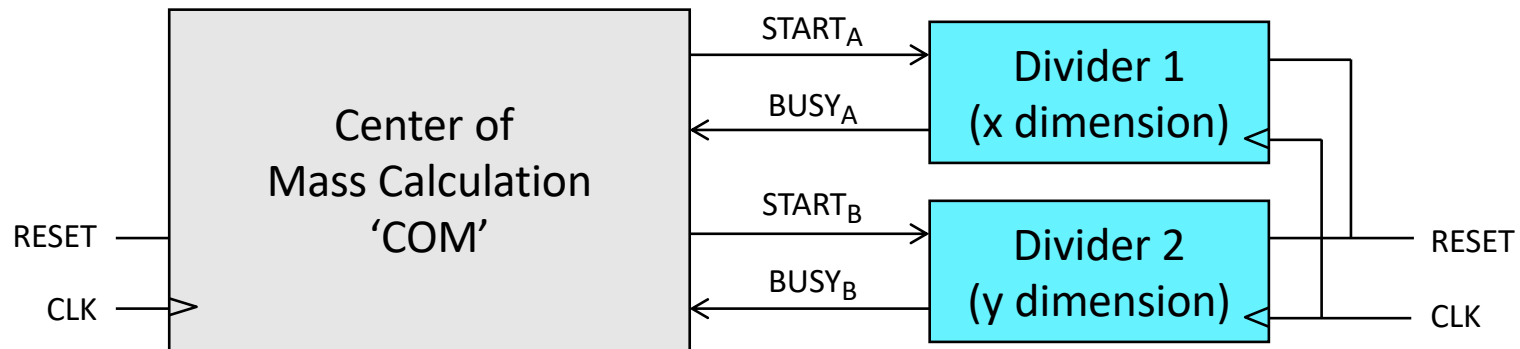


- C.O.M. will be in a “data collection state” during the active portion of a video frame
- When the frame’s active part is done, it needs to calculate the average x,y position of the “hot” pixels it has observed.
- To divide, the C.O.M. module hands the values it needs divided off to two separate dividers.
- C.O.M. waits on them monitoring their BUSY signals
- They can do division separately (in parallel)
- When done, they report back to the C.O.M with their result
- C.O.M. reports to outside world its calculation

One “Bad” Attempt at Division

- In previous lecture looked at *what* this actually builds
- We can ask Vivado to synthesize division logic for us, and it actually will do it.
- This code constrains the act of division to having to exist between two clock edges.:

```
module top_level(  
    input wire clk_100mhz, //clock @ 100 mhz  
    input wire [15:0] sw, //switches  
    input wire btnc, //btnc (used for reset)  
    input wire btnu, //btnc (used for reset)  
    input wire btnl, //btnc (used for reset)  
    output logic [15:0] led //just here for the funs  
);  
    logic old_btnl;  
    logic old_btnu;  
    logic old_btnc;  
    logic [15:0] quotient;  
    logic [15:0] dividend;  
    logic [15:0] divisor;  
    assign led = quotient;  
    always_ff @(posedge clk_100mhz)begin  
        old_btnl <= btnl;  
        old_btnu <= btnu;  
        old_btnc <= btnc;  
    end  
  
    always_ff @(posedge clk_100mhz)begin  
        if (btnc & ~old_btnc)begin  
            dividend <= sw; //divide //load dividend  
        end  
        if (btnc & ~old_btnc)begin  
            divisor <= sw; //divide //load divisor  
        end  
    end  
endmodule
```

Circuit Built:

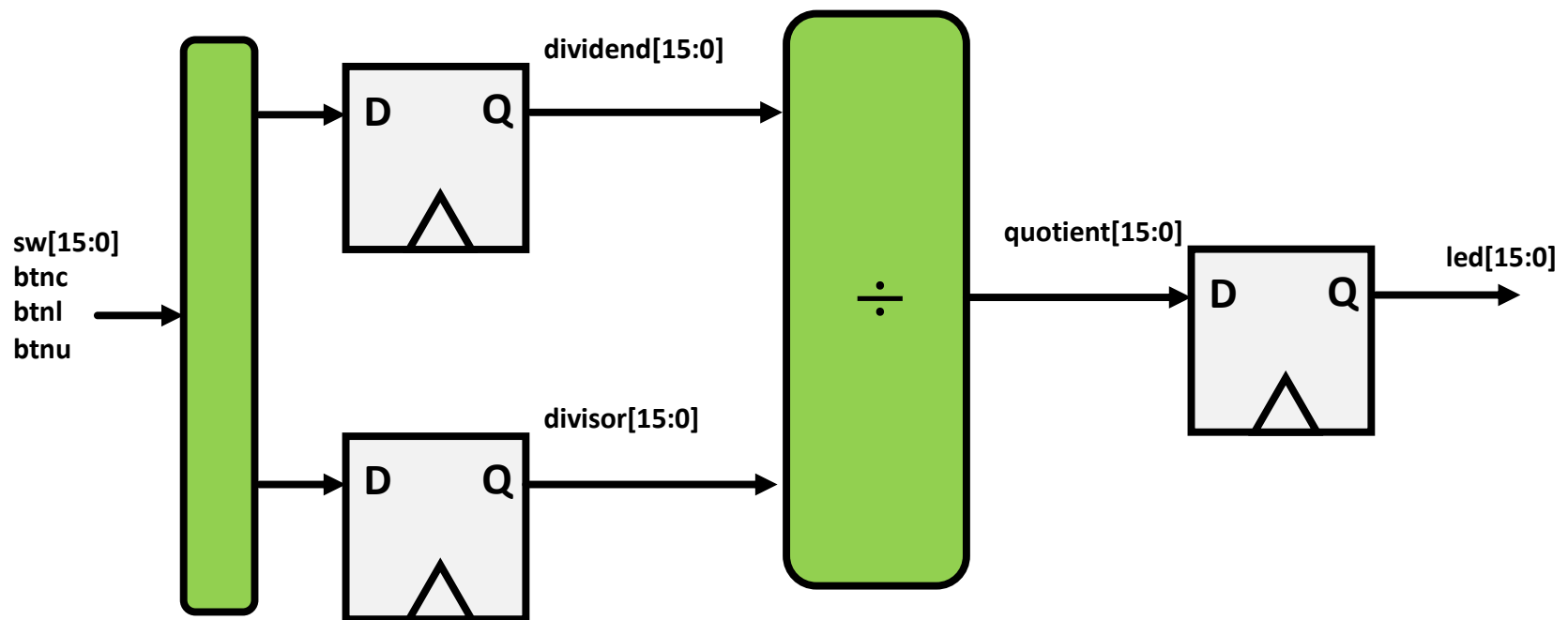

Build the Stupid Divider


Violates timing!

```
Phase 22 Post Router Timing
INFO: [Route 35-20] Post Routing Timing Summary | WNS=-21.399 | TNS=-129.552 | WHS=0.090 |
THS=0.000 |
```

| Site Type | Used | Fixed | Prohibited | Available | Util% |
|--|------|-------|------------|-----------|-------|
| Slice | 100 | 0 | 0 | 15850 | 0.63 |
| SLICEL | 89 | 0 | | | |
| SLICEM | 11 | 0 | | | |
| LUT as Logic | 274 | 0 | 0 | 63400 | 0.43 |
| using 05 output only | 0 | | | | |
| using 06 output only | 274 | | | | |
| using 05 and 06 | 0 | | | | |
| LUT as Memory | 0 | 0 | 0 | 19000 | 0.00 |
| LUT as Distributed RAM | 0 | 0 | | | |
| LUT as Shift Register | 0 | 0 | | | |
| Slice Registers | 55 | 0 | 0 | 126800 | 0.04 |
| Register driven from within the Slice | 16 | | | | |
| Register driven from outside the Slice | 39 | | | | |
| LUT in front of the register is unused | 26 | | | | |
| LUT in front of the register is used | 13 | | | | |
| Unique Control Sets | 4 | | 0 | 15850 | 0.03 |

Now Do same Thing With 32 bits:
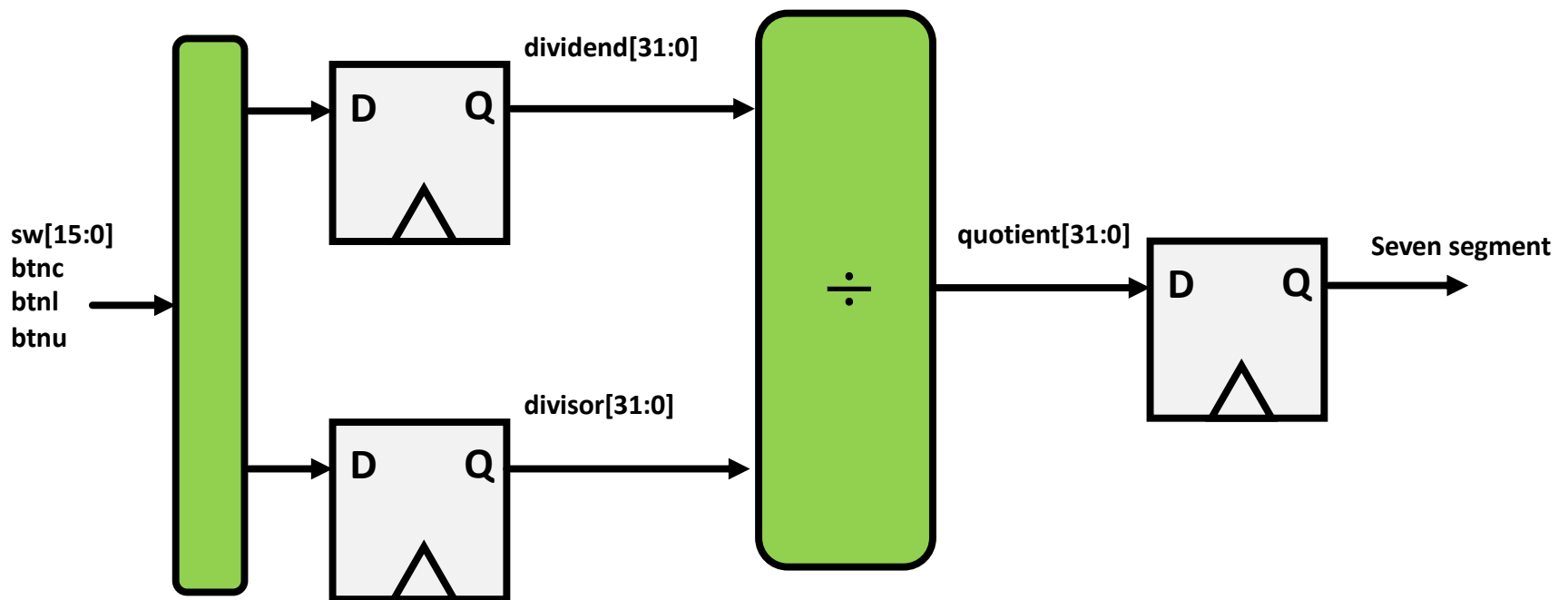
```
if (pmod_pin & ~old_pmod_pin) begin
    quotient <= dividend/divisor;
end
```



**See lecture code for full implementation and build. (divider0)*

Build the Stupider Divider


```
Phase 20 Post Router Timing  
INFO: [Route 35-20] Post Routing Timing Summary | WNS=-72.004| TNS=-1004.354| WHS=0.227 | THS=0.000 |
```

```
Phase 20 Post Router Timing | Checksum: 1d10fc4d8
```

2. Slice Logic Distribution

| Site Type | Used | Fixed | Prohibited | Available | Util% |
|--|------|-------|------------|-----------|-------|
| Slice | 301 | 0 | 0 | 8150 | 3.69 |
| SLICEL | 225 | 0 | | | |
| SLICEM | 76 | 0 | | | |
| LUT as Logic | 944 | 0 | 0 | 32600 | 2.90 |
| using 05 output only | 0 | | | | |
| using 06 output only | 922 | | | | |
| using 05 and 06 | 22 | | | | |
| LUT as Memory | 0 | 0 | 0 | 9600 | 0.00 |
| LUT as Distributed RAM | 0 | 0 | | | |
| LUT as Shift Register | 0 | 0 | | | |
| Slice Registers | 131 | 0 | 0 | 65200 | 0.20 |
| Register driven from within the Slice | 67 | | | | |
| Register driven from outside the Slice | 64 | | | | |
| LUT in front of the register is unused | 28 | | | | |
| LUT in front of the register is used | 36 | | | | |
| Unique Control Sets | 7 | | 0 | 8150 | 0.09 |

A Better Divider?

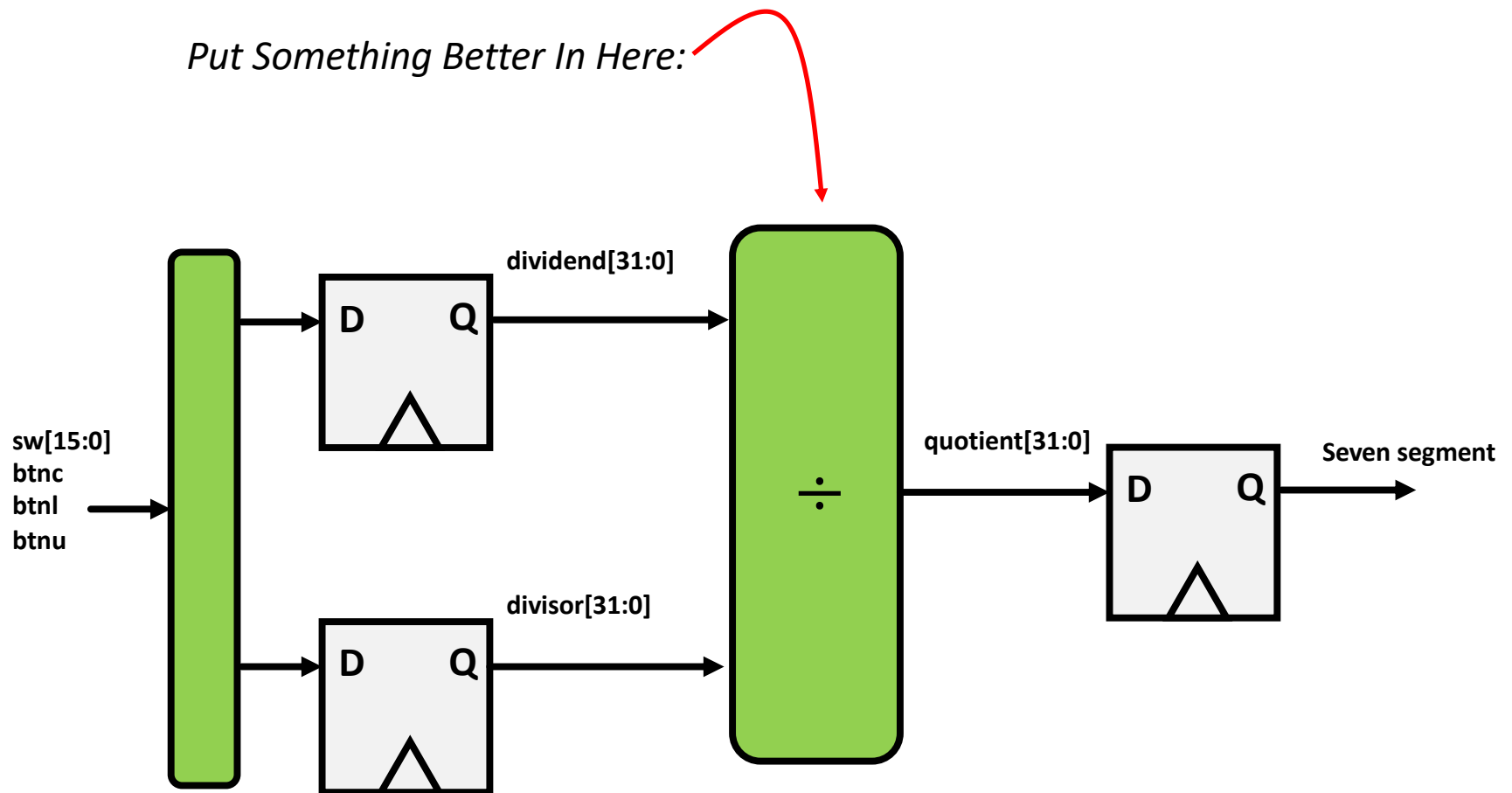

**See lecture code for full implementation and build. (divider0)*

So conclusions

- $+$, $-$, $*$ can be done in a clock cycle with exceptions
- Watch out for flow-control logic...that can start to stack up
- $/$ will never happen in one clock cycle. Accept that.
- Similar other things like square root, cosine, etc...those need clock cycles...or if you absolutely need those in one/two cycles, you do a lookup table of pre-computed values (takes huge amounts of memory)


Back on pipelining...

- If we have time... A white blip
- In lab 05, early on you may see an artifact on popcat



(Two registers coming from delay in memory access/read)

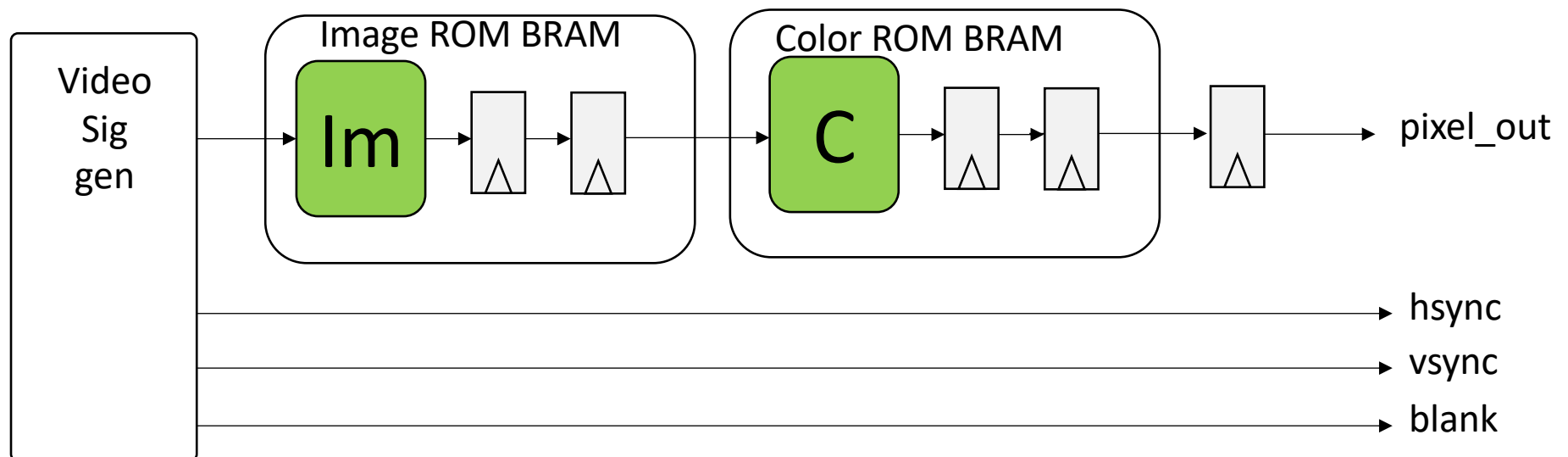
- Monitor drawing based on vsync, hsync, blank,
- But what image rom is giving it is 5 clock cycles behind
- At start of Death Star nothing in the “pipeline” yet



```


1
2 // calculate rom address and read the location
3 assign image_addr = (hcount_in-x_in) + (vcount_in-y_in) * WIDTH;
4 image_rom rom1(.clka(pixel_clk_in), .addra(image_addr), .douta(image_bits));
5
6 red_coe rcm (.clka(pixel_clk_in), .addra(image_bits), .douta(red_mapped));
7
8 always_ff @(posedge pixel_clk) begin
9     if ((hcount_in >= x_in && hcount_in < (x_in+WIDTH)) &&
10         (vcount_in >= y_in && vcount_in < (y_in+HEIGHT))) begin
11         pixel_out <= {red_mapped[7:4], red_mapped[7:4], red_mapped[7:4]}; // greyscale
12     end else begin
13         pixel_out <= 0;
14     end
15 end
16

```

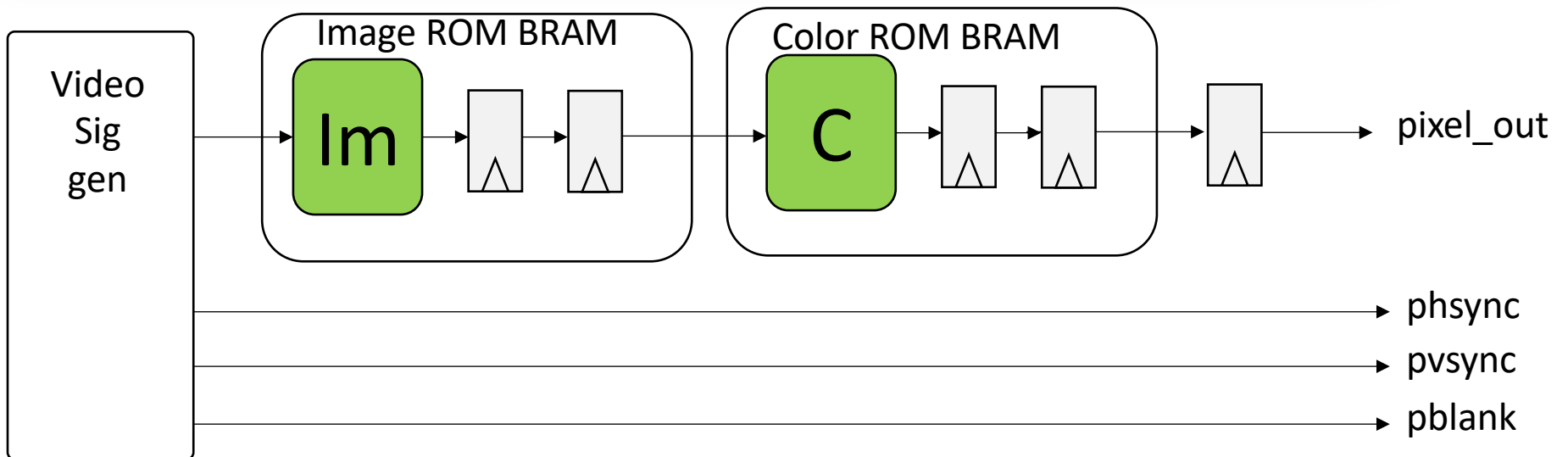

How to Fix?

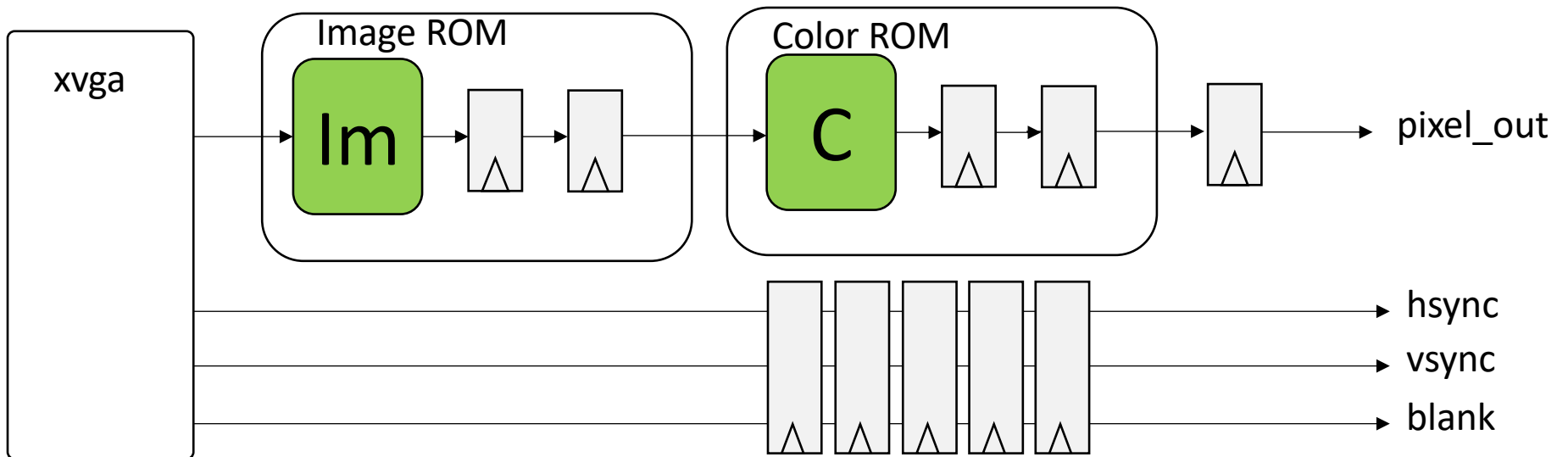- Delay the other signals so everybody is the same



Turn the whole thing into a 5-stage pipeline!

Pipelining

- Pipeline in Verilog!
- Make sure other things are protected too!


```
logic hs_pip[4:0];
logic vs_pip[4:0];
logic b_pip[4:0];

always_ff@(posedge clk_in)begin
    hs_pip[0] <= hsync_in;
    vs_pip[0] <= vsync_in;
    b_pip[0] <= blank_in;
    for (int i=1; i<5; i = i+1)begin
        hs_pip[i] <= hs_pip[i-1];
        vs_pip[i] <= vs_pip[i-1];
        b_pip[i] <= b_pip[i-1];
    end
end
assign hsync_out = hs_pip[4];
assign vsync_out = vs_pip[4];
assign blank_out = b_pip[4];
```

Final Project Ideas

- Things with video and/or related topics are very “relevant” to FPGAs
- You have to move and process very large amounts of data with demanding timing.
- This is something software often cannot do on its own.


Live Pong

 

Glow Trails



DigiEyes

 

Final Project Info released by tomorrow

- Start Teaming!
- Teams of 2 or 3!