

6.205  
(aka 6.111)

# Combinational Logic

Fall 2025

# Administrative

---

- Week 1's content is due tomorrow (Wednesday) night at 11:59pm
- Week 2's content will come out Thursday after lecture @4pm

# Review

---

1. Have an Idea: "I have three wires of one bit,  $x$ ,  $y$ , and  $z$ .
  - I want to treat them collectively as a number...where  $z$  is the one's place,  $y$  is the two's place, and  $x$  is the four's place.
  - If that number is 3, 5, 6, or 7, I want the output bit to be high, else I want it to be low.

*\*"High" and "Low" refer to the two states in the digital domain*

# Review

---

## 2. Implement the idea in SystemVerilog:

```
module some_module
( input wire x,
  input wire y,
  input wire z,
  output logic out);


  logic [2:0] temp;
  assign temp = {x,y,z};
  always_comb begin
    if (temp>=5)begin
      out = 1'b1; //specify bit
    end else if (temp==3)begin
      out = 1'b1; //specify bit
    end else begin
      out = 1'b0; //specify bit
    end
  end
end
endmodule
```

# This Then gets Turned into a Circuit

---

- Most synthesis tools will provide some sort of intermediate visualization if you want.
- Yosys (an open toolchain) can do this somewhat easily.
- This site here: <https://digitaljs.tilk.eu/> is built on Yosys and let's you see what pops out
- For example module from previous page yields...

# Equivalent Schematic

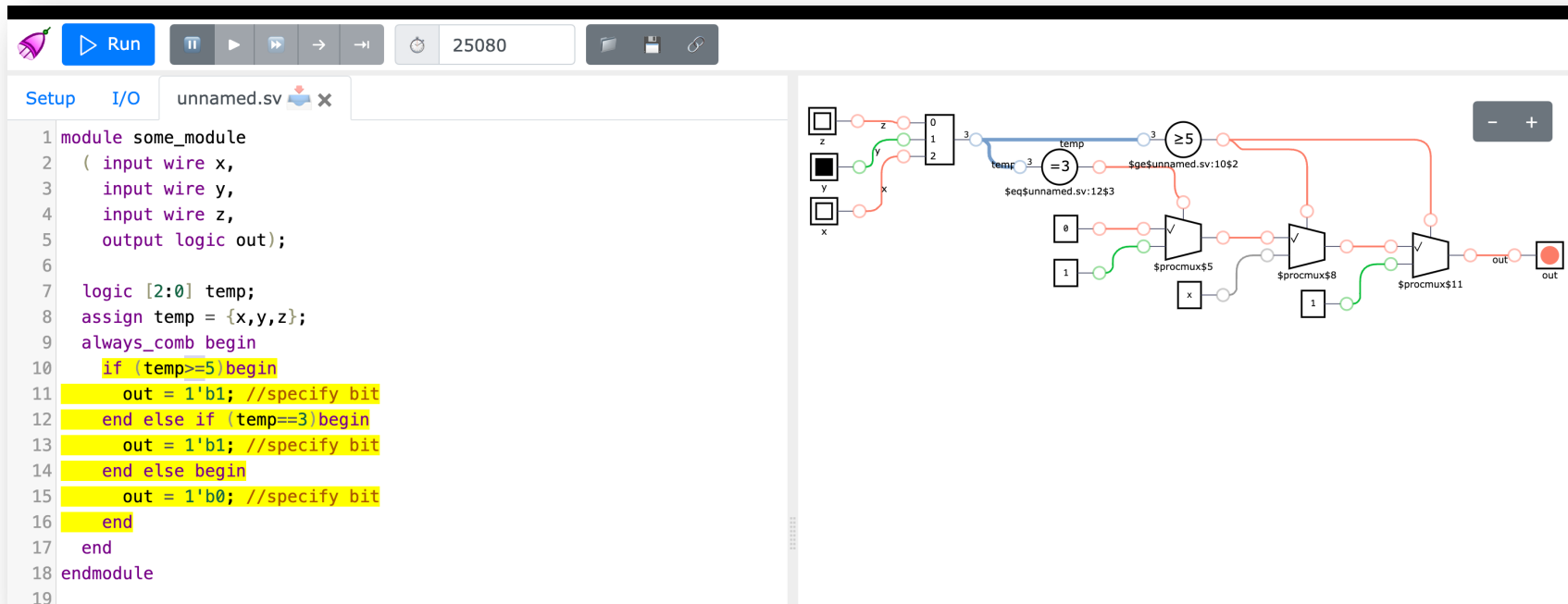

# This can be helpful, but isn't the full story

---

- In reality when this gets built on an FPGA, additional steps will be taken to reduce it into more primitive functional expression, which we can helpfully visualize with a truth table or sum of products.
- For this example, it would look like this:

$x$	$y$	$z$	$output\_1$
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

# Review

---


$x$	$y$	$z$	$output\_1$
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

- These truth tables are important because they are effectively the “code” that are used to program the fundamental units of the FPGA, the CLBs and associated wiring


 
# Xilinx Logic Blocks

- Our FPGAs have about 8500 of these →
- Called “Logic Slices”
- Each slice has four CLBs (“Configurable Logic Blocks”) that form the clay from which we sculpt our digital functions



# Variables in Verilog

---

- We'll use the `logic` type for our basic variable in 6.205
- It can represent a few different things depending on usage:
  - A "wire"...literally the routed output of some logic
  - A "reg"...a device that can hold a value over time (a form of memory)
- Right now we're not super worried about "reg"s

```
logic a; //simple variable (one bit in size)...can only hold 0 or 1
logic a,b,c; //declaring three single bit variables at the same time
```

# There are other Data Types

---

- SystemVerilog the language has other datatypes
- There are int's, shorts, etc...all with signed/unsigned versions...we'll leave them be for a little bit!
- However when we do things with loops we'll use int's to help us iterate!
- For now just use **logic** variables.
  - Can be any size
  - By default unsigned (we'll worry about signed-ness in future weeks)

# Multibits in Verilog

---

- Want variables that can contain more than one bit of information?
- Specify the sizing left-to-right like shown
- Can make any size you want, 2, 11, 17 bits
- Don't feel compelled to use extra bit just because you've heard of variables being 32 bits or 16 bits before. Not bound by that structure.

```
logic [7:0] a; //8bit value (also think of this as an array of 8 bits)
logic [31:0] b; //32 bit value
logic [12:0] c,d; //making two arrays, each 13 bits that called c and d
```

# Arrays in Verilog

---



- Can also make "2D" arrays (packed/unpacked):
- The bottom two arrays are similar, but also different:
  - One is "packed"
  - One is "unpacked"
- Packed dimensions are specified before the variable name
- Unpacked dimensions are specified after the variable name

```
logic [7:0] array3;           //8 bit "packed array"
logic [7:0] array4 [2:0];    //three 8 bit unpacked arrays (b[0] not contiguous with b[1])
logic [2:0][7:0] array5 ;    //three 8 bit packed arrays
                             //(array5[0] contiguous with array5[1])
```
  
# Un/Packed Arrays

- Packed means:
  - Whole structure is continuous
  - Like a subdivided larger array
- Unpacked means:
  - Separate/not continuous

```
logic [7:0] array3;           //8 bit "packed array"  
logic [7:0] array4 [2:0];    //three 8 bit unpacked arrays (b[0] not contiguous with b[1])  
logic [2:0][7:0] array5 ;    //three 8 bit packed arrays  
                             //(array5[0] contiguous with array5[1])
```





# Un/Packed Arrays

- Packed/Unpacked has little meaning beyond the program construct within the Verilog language

```
logic [7:0] array3;           //8 bit "packed array"  
logic [7:0] array4 [2:0];    //three 8 bit chunks (unpacked)  
logic [2:0][7:0] array5 ;    //really just one 24-bit chunk with sub-indexing convenience
```

  - Unpacked array: Use to handle the output of three separate adders, for example
- Packed array: Use to represent a string type object, for example (maybe?).



# Get familiar with the Three Bases

---

- Get somewhat fluent with the three bases.
- It will make life easier!

Denary	Binary	Hex
0	0000	0
1	0001	1
2	0010	2
3	0011	3
4	0100	4
5	0101	5
6	0110	6
7	0111	7
8	1000	8
9	1001	9
10	1010	A
11	1011	B
12	1100	C
13	1101	D
14	1110	E
15	1111	F



# Values in Verilog

---

- Good practice to always specify values in the following form: `S'Txxxx_xxxx` where
  - `S` is the size of the number (in bits)
  - `'` is the single quote marker
  - `T` is the numerical base you're specifying the value in
    - `b` for binary (0,1)
    - `d` for decimal (0,1,2,3,4,5,6,7,8,9)
    - `h` for hex (0,1,2,3,4,5,6,7,8,9,A,B,C,D,E,F)
  - `xxxx_xxxx` are your values
    - The `_` is ignored in evaluation
    - use `_` to make more readable
    - Don't need to use `_` but is really nice

# Values in Verilog

---

- Some examples:

```
10'b0101_0101_00; //10 bit size of value...
10'b1; //10 bit value but only lsb specified...so this is saying 10'b0000_0000_01;
12'hF0F; //12 bits..this would be 12'b1111_0000_1111;
9'hF0F; //9 bits so 9'b1_0000_1111; top three cut off since we said only 9 long
15; //assumed to be an 32 bit integer by default:
    //          'b0000_0000_0000_0000_0000_0000_1111;
```

# Assignments

---

- Consider these:

```
logic a, b, c, d, e;  
assign a = 1'b1; //best practice shows you mean to make this 1 bit  
assign b = 0;  
assign c = 1;  
assign d = 15;  
assign e = a && b;
```

- What values will all five variables have?

# Assignments II

---

- What about arrays?

```
logic [7:0] a, b, c;  
assign a = 8'b1010_1010; //good!  
assign b = 16'hF0F0; //fine, but the top eight bits won't get stored  
assign c = 32; //fine, but has: 8'b0010_0000 in it (surprise?)
```

- Watch out for size!
- Arrays have a size...you try to fit something too large in...it will get cut off (lsb's will get preference)

# Assignments III

---

- What if we'd like to merge arrays?:

```
logic [7:0] a, b, c;
assign a = 8'b1010_1010; //good!
assign b = 16'hF0F0; //fine, but the top eight bits won't get stored
assign c = 32; //fine, but has: 8'b0010_0000 in it (surprise?)
logic [15:0] d;
logic [7:0] e, f;
assign d = {a,b}; //16'b1010_1010_1111_0000
assign e = {a[3:0], b[3:0]}; //has 8'b1010_0000;
assign f = {a,b}; //will have: 8'b1111_0000;
```

- Index into them however you want

# Assignments IIb

---

- What about this?

```
logic [2:0] e;  
assign e = {1,1,1};
```

# Other Ways to Assign (Implicit)

---

- Can also assign values upon declaration of variables in Verilog (implicit declaration as opposed to explicit with the assigns):

```
logic a = 1'b1; //same as assign a= 1'b1;  
logic b = 1'b0;  
logic [3:0] c = 4'b1010;
```

*I'd generally recommend against doing this! Because...*

```
logic [3:0] d = 4'b1100;  
assign d = 4'hF;  
//might error out...might "choose for you"
```

- Be careful! Can't assign twice! This is not software! Higher up on page does not necessarily mean "earlier"

# Other Ways to Assign (always\_comb)

---

- You can also assign values/set relationships inside of a block known as `always_comb`
- Don't need to use `assign` in `always_comb`:

```
logic a, b, c;

assign a = 1'b1;
assign b = 1'b0;
assign c = a^b;

//alternatively could do:
always_comb begin
    a = 1'b1;
    b = 1'b0;
    c = a^b;
end
```



# Why Use an always\_comb?

---

- Can let you be more expressive, particularly when more complicated relationships need to be expressed!
- For example, can now do if/else logic cleanly

```
logic [3:0] a, b, c; //three four bit values!
always_comb begin
    if (a==4'b1010)begin
        c = 4'b1; //(0001)
    end else if (b==4'b0000)begin
        c = 4'b1010;
    end else begin
        c = 4'b0000;
    end
end
```

# Why Use an always\_comb?

---

- Always-family blocks also are analyzed *in order* if you use (=) assignments...Example:

```
logic [3:0] a, b, c; //three four bit values!
always_comb begin
    a = 4'b1010;
    a = a+b;
    a = a+c;
end
```

- Is the same as:

```
assign a = 4'b1010 + b + c;
```

# Inside an always-type block

---

- Order of Code *\*can\** matter

```
logic [3:0] a, b, c; //three four bit values!
always_comb begin
    a = 4'b1010; //this line evaluated first!
    a = a+b; //this line evaluated second!
    a = a+c; //this line evaluated third!
end
```

- The entire block is analyzed and turned into a “hidden” one-liner like this\*:

```
assign a = 4'b1010 + b + c;
```

*\*or something...differences aren't important now.*

# Case Statement

---


- Need to do in an always block:

```
logic [8:0] a;
logic [1:0] b;
//make b 0, if a is 'b1111_0000
//make b 1, if a is 'b1010_0001
//make b 2, if a is 'b0000_1000
//else b is 3
always_comb begin
    case(a)
        8'hF0 : b = 2'b0;
        8'hA1 : b = 2'b1;
        8'h08 : b = 2'b10;
        default : b = 2'd3;
    endcase
end
```

- Use these in place of long-chained if/else statements that are checking same variable
- **Always have a default case! (safe, good practice)**
- There is no fall-through in Verilog (no need for break statements like in C/C++)
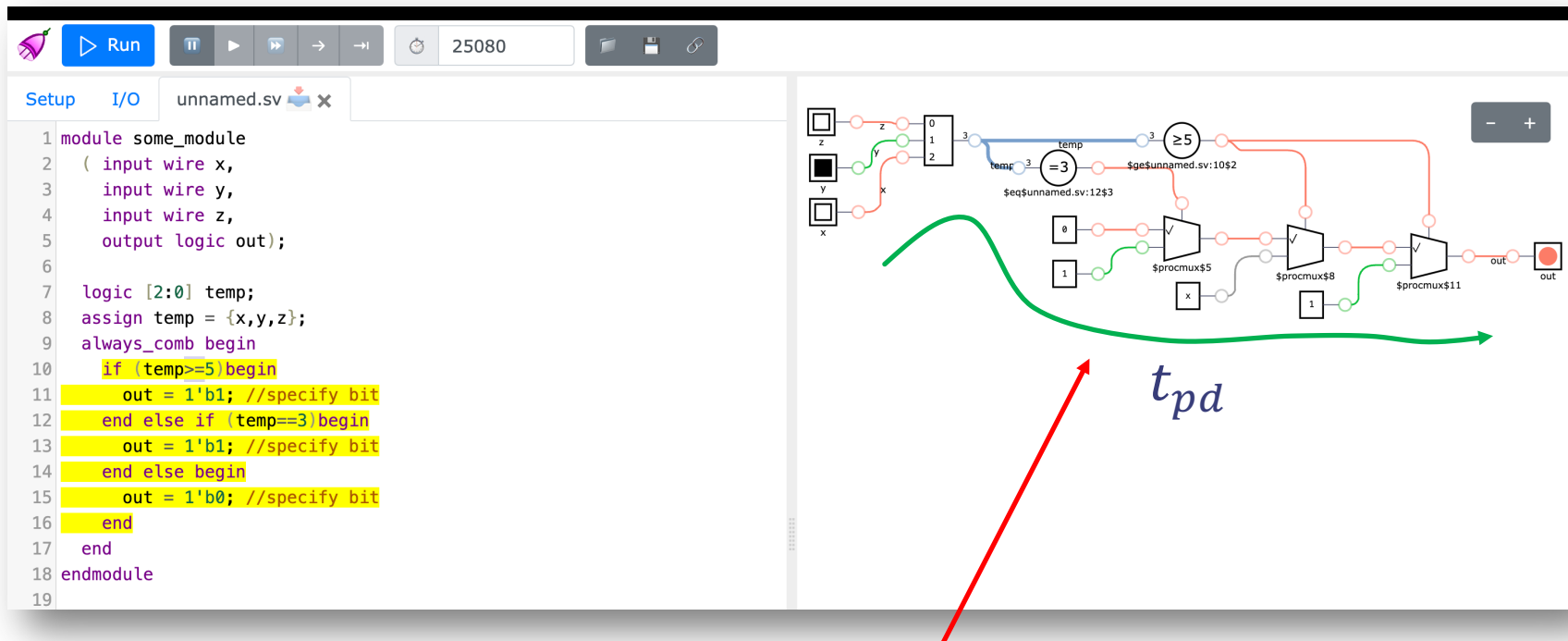
# Why Try to Avoid Long-Chained If-Else?


- Because if, else if, else if, else... has a priority encoded in it....a hierarchy of when one decision should be made relative to others.



*Can end up having a loooong propagation delay*
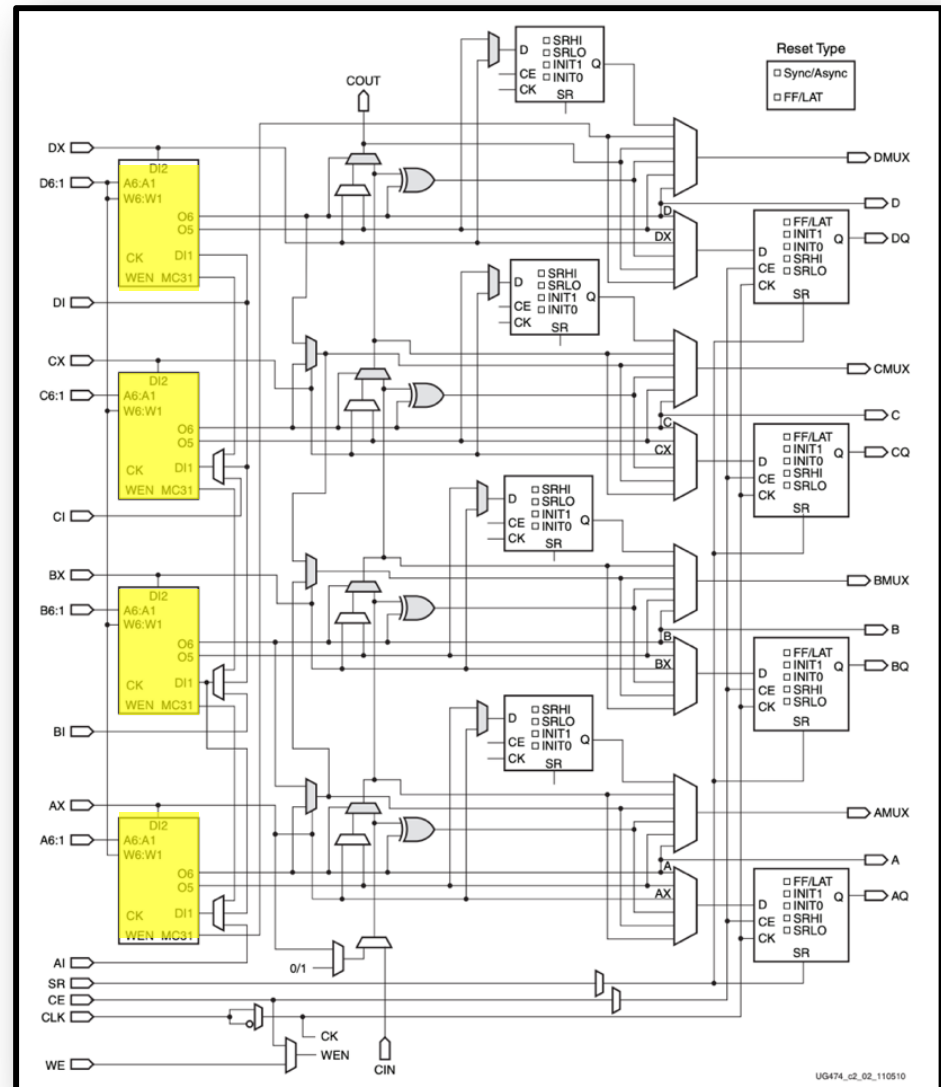
# Case Statements

- Can evaluate to multi-bit multiplexers which are relatively “shallow” pieces of logic with lower propagation delays
- And readily available in FPGA:
- More on Thursday



# Always blocks?

---

- For stuff you write, stick with specific always family blocks:
  - `always_comb`
  - `always_ff` (coming up)
  - `always_latch` (coming up)

# What about always @(\*)

---

- Historically, there was just one always block and you would infer different types of logic (combinational, latch, or sequential) from what was in the parentheses:

```
always @(<sensitivity list>)begin  
  
    //do your stuff here when a change happens  
    //to anything specified in sensitivity list  
  
end
```




# Simple combinational adder

---

- For example you would do:

```
always @(x,y)begin
    z= x+y;
end
```


*"any time x or y changes, z changes as x+y." This is a purely combinational adder*



- Verilog 2001 brought in the "wildcard". Same as above can be done with:

```
always @(*)begin
    z= x+y;
end
```

*"any time anything in the block changes, z changes as x+y." This is a purely combinational adder*



# Consider This Situation

---

- “I want a combinational circuit that says  $z = x+y$  if  $x$  is 3.”
- Here's my solution:

```
always @(*)begin
    if (x==3)begin
        z = x+y;
    end
end
```

- Problems with this?

# Remember what we're doing

---

- We are specifying (using HDL) a Boolean function. That function has a finite input space.
- We need to make sure we are specifying how this circuit should work for the *entire* input space:

```
always @(*)begin
    if (x==3)begin
        z = x+y;
    end
end
```

- Code above is saying set z to be x+y when x==3. It says nothing else.
- There is a device that will enable this as stated but it is not combinational!

# The Resulting Truth Table

---

- Let's just assume  $x$  is two bits...

$x[1]$	$x[0]$	$f(x, y, z)$
0	0	?
0	1	?
1	0	?
1	1	$x + y$


- Not to decide is to decide...
- What you just want it stay the same or something?  
That's opening up a whole world of issues...  
Staying the same means you need a concept of time in your truth table...

# A part that remembers (starting in Lec 03)

- Talked a little about stateful things in lecture 1... in addition to combinational blocks there are several stateful things too!
- Two big ones!

## D Latch


*Level-Triggered Sample-and-Hold Device*

 

*"store D when E is high"*

## D Flip-Flop

*Edge-Triggered Sample-and-Hold Device*

 

*"store D when clk rises"*

# Missing Input Space

---

```
always @(*)begin
    if (x==3)begin
        z = x+y;
    end
end
```

- This code fails to specify what to do when  $x \neq 3$ .
- It therefore assumes you want to do nothing.
- A latch will do that:
  - When  $x == 3$ , set  $z$  to be  $x+y$
  - When  $x \neq 3$ , hold the value you already have
- Correct code would be:

```
always @(*)begin
    if (x==3)begin
        z = x+y;
    end else begin
        z = 0;
    end
end
```

# A latch is not combinational

---

- Suddenly your design will have “memory” in it where you never intended.
- This can mess up your simulations and designs!
- Vivado will happily synthesize a latch for you since it'll think that's what you want.
- Forcing it to know you want combinational logic (via `always_comb`) can throw warnings:  

```
WARNING: [Synth 8-327] inferring latch for variable  
'z_reg' [/top_level.sv:12]
```
- It will also ensure there's less chance of simulation-to-reality variations

# To be annoying!!!!

---

- We are specifying (using HDL) a Boolean function. That function has a finite input space.
- We need to make sure we are specifying how this circuit should work for the **entire** input space:
  - Ideally do this explicitly
  - If you do implicitly make sure you're doing so responsibly!
- If you fail to specify your truth table in full, unknown behaviors will exist and wreak havoc

<i>x</i>	<i>y</i>	<i>z</i>	<i>output_1</i>
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	?
1	1	0	?
1	1	1	?



# Never use `always`

# Always use `always_comb`

---

- When writing your logic:
  - Make sure to cover the entire input space for each variable in its entirety!
  - Do not forget about leftovers:
    - Have a terminal else in case of if/else if chain
    - Have a default case in the case of a case statement
    - Initialize starting values for variables at start of `always_comb` block!
  - Scan output logs from vivado for word “latch”. If there’s any getting inferred, make sure it is because you want them (very unlikely in our class)

# In Conclusion

- Tons of legacy code will have them so you should be aware and know how to how to read it and deal with it!

No way ~~drugs~~ **always@()** blocks are for loserzz! I've got too much to lose to get mixed up with them.



- For stuff you write, stick with specific always family blocks:
  - `always_comb`
  - `always_ff` (coming up)
  - `always_latch` (coming up)

# Other Syntax...Ternaries

---

- See these a lot in Verilog
- One-line if/else/if chains done on right side of assignment:

```
logic [1:0] a, b;
```

```
a = b==2'b11? 2'b0: 2'b10;
```

a is

if b==2'b11:  
a is 2'b0

else a  
is 2'b10

# Ternaries

---

- Can also be done outside `always_comb` in regular assignment statements:

```
logic [1:0] a, b;  
assign a = b==2'b11? 2'b0: 2'b10;  
//if b is 2'b11, a is 0, else it is 2'b10
```

# Ternaries

---

- Can also chain ternaries

```
always_comb begin
  if (a==4'b1010)begin
    c = 4'b1; //(0001)
  end else if (b==4'b0000)begin
    c = 4'b1010;
  end else begin
    c = 4'b0000;
  end
end
```

- Is the same as:

```
logic [3:0] a, b, c; //three four bit values!
assign c = a==4'b1010 ? 4'b1 : b==4'b0000 ? 4'b1010 : 4'b0000;
```

- Or since we're in a C-style language:

```
logic [3:0] a, b, c; //three four bit values!
assign c = a==4'b1010 ? 4'b1
          : b==4'b0000 ? 4'b1010
          : 4'b0000;
```

# Ternary style Specification

---

- One benefit of it is that by its syntactic nature it forces you to have a trailing else:

```
logic [1:0] a, b;  
assign a = b==2'b11? 2'b0: 2'b10;  
//if b is 2'b11, a is 0, else it is 2'b10
```

- You cannot have something like this:

```
logic [1:0] a, b;  
assign a = b==2'b11? 2'b0;  
//if b is 2'b11, a is 0
```

- Nice because it forces you to cover your full input space of possibility, avoiding gaps/resulting latch

# Competing Assignments

---

- What if I have two always\_comb blocks?

```
always_comb begin
    a = c + e;
end

always_comb begin
    a = d + 5;
end
```

- Only one will be chosen, the other ignored. It will not make a union or merge the two.

# Multiple always-type blocks

---

- It is fine to use values across multiple always blocks or continuous assign statements, but you should only specify them in one and only one location!

```
always_comb begin
    d = a + 5;
end

always_comb begin
    b = a + 8;
end
```

- Specifying/assigning a variable in multiple always-type blocks is a no-no however



# Where to Create Variables

---

- Variables are things that exist physically
- Always blocks are meant to describe action.
- You *can never* declare variables in an always block
- As much as possible try to declare at top (with nice comments)
- And implement logic (assign, always\_comb, etc) below it

# Parameters

---

- Parameters are different than variables.
- Their values can change, but only at the compile-stage.
- At run-time they are constants.
- They allow us to make flexible designs (make an adder that can be 8 bits or 14 bits or whatever)

# Parameters

---

- Parameters allow us more flexibility in programmatically describing our designs:

```
localparam GOOD = 8'b1111_1111; //not changeable
localparam STATE_SIZE = 8;
parameter BAD = 8'b1111_0000; //changeable (see in a few slides how/where)
logic [STATE_SIZE-1:0] state; //made size of state variable based on param
logic [1:0] output;
always_comb begin
    case(state)
        GOOD : output = 2'b11;
        BAD : output = 2'b00;
        default : output = 2'b10;
    endcase
end
```

Apply more meaningful names to values in certain contexts of program

Allow us to describe variable attributes using common adjustable values

# Parameters

---

- `localparam` is local to the module it exists in
- `parameter` is local, but (depending on context), can be a configuration setting (see in a minute)
- Always CAPITALIZE so they are easy to spot
- Parameters can be based on other parameters!

```
parameter NUM_CHICKENS = 167;  
parameter CHICKEN_WIDTH = $clog2(NUM_CHICKENS);  
logic [CHICKEN_WIDTH-1: 0] chicken_counter;
```

- `$clog2` is a Verilog math operator run at compile time
- Other Verilog math functions here:  
<https://www.chipverify.com/verilog/verilog-math-functions>

# Modules

---

- Just like the idea of functions in software! Wrap up functionality in a reusable and “instantiable” blob

```
module not_gate (input wire x, output logic y);  
    assign y = !x;  
Endmodule  
  
module main_module();  
    logic a,b;  
    assign a = 1'b1;  
    not_gate ng1 (a,b);  
endmodule
```

Specify  
input/output  
variables and  
attributes  
(like size)

Do your operations

//ng1 is name of instance

Make an instance of your module  
(name it) and use it

Declare instance like: `module_name instance_name (arg0,arg1,...);`

# Modules...but you really should use named port convention!

---

- Just like the idea of functions in software! Wrap up functionality in a reusable and “instantiable” blob

```
module not_gate (input wire x, output logic y);  
    assign y = !x;  
Endmodule
```

Specify  
input/output  
variables and  
attributes  
(like size)

Do your operations

```
module main_module();  
    logic a,b;  
    assign a = 1'b1;  
    not_gate ng1 (.x(a), .y(b));  
endmodule
```

//ng1 is name of instance

Make an instance of your module  
(name it) and use it

# Parameterized Modules

---

- We mentioned parameters previously. They can be used to make flexible modules:

```
module add_constant #(parameter T0_ADD = 12)
    (input wire [7:0] val_in, output logic [7:0] val_out);
    assign val_out = val_in + T0_ADD;
endmodule

module top();
    logic[7:0]a,b,c,d;
    assign a = 8'd11;
    assign c = 8'b100;
    add_constant ac_0 (.val_in(a), .val_out(b));

    add_constant #(.T0_ADD(5)) ac_1 (.val_in(c), .val_out(d));
    //value of b?
    //value of d?
endmodule
```

# Parameterized Modules

---

- Parameterizable modules are more complicated to write, but their reusability is a great feature
- If a parameter is not specialized upon instantiation, the default is used instead.
- Parameters can be used to specify other parameters in the design!



# Operator Precedence

- Largely borrowed from C!
- Be careful some of these often feel out of order for people.
- Left/right shift for example!
- For example if:
  - $x=100$
  - $q=8$
  - What will  $y$  be?

`assign y = x + q>>2;`

- 27...not...102

Verilog Operator	Name	Functional Group
[ ]	bit-select or part-select	
( )	parenthesis	
!	logical negation	logical
~	negation	bit-wise
&	reduction AND	reduction
	reduction OR	reduction
~&	reduction NAND	reduction
~	reduction NOR	reduction
^	reduction XOR	reduction
~^ or ^~	reduction XNOR	reduction
+	unary (sign) plus	arithmetic
-	unary (sign) minus	arithmetic
{ }	concatenation	concatenation
{ { } }	replication	replication
*	multiply	arithmetic
/	divide	arithmetic
%	modulus	arithmetic
+	binary plus	arithmetic
-	binary minus	arithmetic
<<	shift left	shift
>>	shift right	shift
>	greater than	relational
>=	greater than or equal to	relational
<	less than	relational
<=	less than or equal to	relational
==	logical equality	equality
!=	logical inequality	equality
===	case equality	equality
!==	case inequality	equality
&	bit-wise AND	bit-wise
^	bit-wise XOR	bit-wise
^~ or ~^	bit-wise XNOR	bit-wise
	bit-wise OR	bit-wise
&&	logical AND	logical
	logical OR	logical
?:	conditional	conditional

# Reduction Operators in Verilog

- Reduction operators act like their bitwise cousins, but are done on a variable rather than between several:

```

logic [7:0] b, d;
logic      a, c;

assign a = |b; //if anything in b is 1, a is 1
assign c = &d; //everything in d needs to b 1
//four others xor and xnor are particularly
useful
    
```

Verilog Operator	Name	Functional Group
[ ]	bit-select or part-select	
( )	parenthesis	
!	logical negation	logical
~	negation	bit-wise
&	reduction AND	reduction
	reduction OR	reduction
~&	reduction NAND	reduction
~	reduction NOR	reduction
^	reduction XOR	reduction
^~ or ^~	reduction XNOR	reduction
+	unary (sign) plus	arithmetic
-	unary (sign) minus	arithmetic
{ }	concatenation	concatenation
{ { } }	replication	replication
*	multiply	arithmetic
/	divide	arithmetic
%	modulus	arithmetic
+	binary plus	arithmetic
-	binary minus	arithmetic
<<	shift left	shift
>>	shift right	shift
>	greater than	relational
>=	greater than or equal to	relational
<	less than	relational
<=	less than or equal to	relational
==	logical equality	equality
!=	logical inequality	equality
===	case equality	equality
!==	case inequality	equality
&	bit-wise AND	bit-wise
^	bit-wise XOR	bit-wise
^~ or ^~	bit-wise XNOR	bit-wise
	bit-wise OR	bit-wise
&&	logical AND	logical
	logical OR	logical
?:	conditional	conditional

# for loops

---

- For loops (and to a lesser extent while loops) exist in Verilog to more conveniently lay out our hardware.
- They are NOT for loops “in time”. They are for loops “in space”
- There are two general types:
  - Generate for loops (for loops in a generate block)
  - Regular for loops
- Which one works can be confusing\* so we'll over it here

\*the rules have also changed as Verilog evolved so there can be confusing info on the internet

# Regular for loop

---

- If you are in an always block and just need to replace a bunch of repetitive lines, a for loop can help
- Let's say I had to do some annoying operation a bunch of times with some variables:

```
logic [7:0] b [63:0];  
logic [7:0] c [63:0];  
logic [63:0] a;  
  
//assume b and c are large enough  
always_comb begin  
    for(integer i =0; i<64; i= i+1)begin  
        a[i] = b[i]>c[63-i];  
    end  
end
```

# Generate for loops

---

- Put a for loop in a **generate** block.
- Use this any time you need to :
  - create multiple assign statements
  - Create multiple `always_comb`, `always_ff` blocks
- OR:
  - Create multiple instances of a module
  - Create logics
- Need to use a **genvar** for your iterating variable rather than an integer.
- Can also label your for loops to have access the modules or entities created within

# Generate For Loops

---

## An Example:

```
generate
  genvar i;
  for(i=0; i<5; i=i+1)begin: myloop
    logic[31:0] hi;
    assign hi = 32'hAAAAAAAA ^ i;
  end
endgenerate
//outside of generate, those logics can be accessed with:
// myloop[2].hi for example
// this is needed since the logic hi needs more
// specificity than provided otherwise.
```

# Rule about For Loops

---

- Inside an `always_comb` (or `always_ff`?):
  - Use *regular for loop*
- Want to make multiple assign statements? Or Multiple `always`-type blocks? or multiple modules?:
  - Use a *generate loop*!
- In both instances, the iterating variables of the loop have no intrinsic hardware meaning...they exist as a helper variable during specification (a copy-paster thingie)

# wire vs. logic. vs. reg

---

- **wire** Can only be signal flow ("nets"). From perspective of a module, signals coming into module are conveyed by wires. In other usage, declared wires can only be given values with **assign** statement. A wire can also be associated with combinational logic.
- **reg** Ideally represents a flipflop or latch (storage mechanism), but in reality can also turn into a net (in other words a wire)/ combinational logic based on usage (cover more on Thursday in Lec 03). Only given values with **always-family** blocks. **DO NOT USE IN 6.205**
- **logic** Can represent all datatypes. Its usage dictates what it ultimately represents (combinational logic or Flip Flops). Can be worked with **assign** and **always-family** blocks



# Why logic?

---

- In addition to allowing us to just use one general type rather than two, the **logic** datatype has stricter protections against multi-driven nets

```
module thing(input wire [3:0] a,b,
output wire [3:0] c);
    //some behavior goes here
endmodule

module main_module();
    logic[3:0] a,b,c;
    thing my_thing(.a(a), .b(b), .c(c));
    assign c = 4'b1010; //whoops might miss checks in Vivado (multi-driven net)
endmodule
```

- Logic on output should prevent:

```
module thing(input wire [3:0] a,b,
output logic [3:0] c);
    //some behavior goes here
endmodule

module main_module();
    logic[3:0] a,b,c;
    thing my_thing(.a_in(a), .b_in(b), .c_in(c));
    assign c = 4'b1010; //should get caught on synthesis
endmodule
```

# So why still use `wire` in module definitions at all?

---

```
module thing(input wire [3:0] a_in,  
             input wire [3:0] b_in,  
             output wire [3:0] c_out);  
    //stuff  
endmodule
```

- Seems excessive...Let's just use logic for everything.
- We would...but...
- This is a thing we do in 6.205 to help us with our Vivado toolchain since it is a picky, picky child.

# If we had a module definition like this:

---

```
module thing(input logic [3:0] a,  
             input logic [3:0] b,  
             output logic [3:0] c);  
    assign c = a ^ b;  
endmodule
```

- This would run just fine in all honesty.
- In the scope of this module, what logic “is” isn’t specified, but by default Verilog interpreters tend to assign the “wire” attribute to unspecified things (like these logic’s would be).

# The Problem...

---

```
module thing(input logic [3:0] a,  
             input logic [3:0] b,  
             output logic [3:0] c);  
  
    assign d = 4;  
    assign c = a ^ b ^ d;  
endmodule
```

- This verilog will synthesize perfectly happy for the same reason the verilog on the previous page did. Why???
- d is undeclared, but Verilog just assumes it is a “wire” by default...a one-bit wire. omg why.

# To Protect Ourselves...

---

- we will (and should) often add the a directive at the top of our file to protect against this:

```
`default_nettype none
```

- This forces Verilog to treat everything not explicitly declared as a none entity and working with those **will** throw an error

# The downside of that though...

---

- All inputs and outputs are of type `logic`
- A `logic` is an abstract type whose physical realization is determined through usage.

```
`default_nettype none
module thing(input logic [3:0] a,
             input logic [3:0] b,
             output logic [3:0] c);
    assign c = a ^ b;
endmodule
```

- In the scope of this module, how these inputs should get their values is never specified so their actual manifestation is left undefined and defaults to a none and an error gets thrown (good!)

# So must make the inputs into wires

---

- All inputs are now wires

```
`default_nettype none
module thing(input wire [3:0] a,
             input wire [3:0] b,
             output logic [3:0] c);
    assign c = a ^ b;
endmodule
```

- In the scope of this module, inputs a and b are explicitly known to be wires (things that convey signals) so there's no ambiguity
- Still have that great protection against accidental variables since they'll be none!

# But That's Not Enough

---

- It just keeps going...
- A lot of Vivado's source files and modules *rely* on the default nettype being wire (I know who would do that?).
- So after our module we need to set things back to defaulting to wire
- So we'll tack this on at the end of files:

```
`default_nettype wire
```



# To Satisfy All of These Issues

---

- Declare inputs to a module as wires since it will fully specify what they are
- Begin and end all modules with nettype compiler directives. This will protect you from implicit declarations by Vivado

```
`default_nettype none
module thing(input wire [3:0] a,
             input wire [3:0] b,
             output logic [3:0] c);
    assign c = a ^ b;
endmodule
`default_nettype wire
```

# Kind of Annoying

---

- Yeah it is. :/ But this is the sort of thing you deal with when working with a large vendor's toolchain.
- Or a language that just can't let go of the past and keeps maintaining various degrees of backwards compatibility back to the 1980s

# Let's build some different adders

---

- Adder 1 (parameter practice):
  - Add up two variable width values (width is parameterized)
- Adder 2: A parameterized adder module that works for an arbitrary bit width and an arbitrary number of input values
- Adder 3/if time...(to get some generate practice):
  - Explicitly lay out a tree-shaped adder module for 8, 8-wide inputs.
  - Force the structure to be a tree shape: